

TFE4520 PROSJEKTOPPGAVE

REPORT

PORTABLE AND RELIABLE DRSSTC  
DEMONSTRATOR  
BY  
ØYSTEIN SMITH

DECEMBER 19, 2016



FACULTY OF INFORMATION TECHNOLOGY, MATHEMATICS AND ELECTRICAL  
ENGINEERING  
NORWEGIAN UNIVERSITY OF SCIENCE AND TECHNOLOGY

POR TABLE AND RELIABLE DRSSTC  
DEMONSTRATOR

## **Abstract**

Universities, knowledge centers and other institutions has the need for equipment that demonstrates physical phenomena in interesting and audience friendly ways. An example of this is a Double Resonant Solid State Tesla Coil (DRSSTC). It is desirable that the instrument is portable, reliable, and safe to use.

The system should take audio as input and output acoustic audio by means of an high voltage electric discharge in air creating plasma (streamer) by the means of a resonant transformer (tesla coil). The system should also be designed such that it will always be functional, and in the case of the system not being functional should fail in a safe and non-destructive way (safe having priority over non-destructive). As well as indicating which part of the system is non-functional. The system should also be designed in such a way that this non-functioning part may be swapped for a spare functioning part. This was achieved with implementing a back plane architecture with detection of if modules are present, and signals that can be used by modules to report errors.

Before any improvements the system had a probability of failure  $P(F)=0,71$ . After improvements we have removed F0 and F9 from the general fault tree, and F2, F3 from the destructive fault tree (F8) and the probability of failure is reduced to  $P(F)=0,18$ . The probability for destructive failure  $P(F_8)$  is reduced from 0,67 to 0,10.

The existing circuit design and implementation had problems with reliability. The reliability of the system was calculated by the use of a source tree based on logged faults to  $P(F)=0,71$ . After implementing a back plane design, and adding carrier wave detection on the input signal the reliability increased to  $P(F)=0,18$ . The probability of destructive failure was reduced from 0,67 to 0,10. This is a large increase in reliability. Portability was present in the existing implementation, and has been increased by removing failure sources that occurred when moving the system.

## Preface

Omega Verksted has a long tradition with providing Tesla Coil shows for the line union 'Omega' and for other student societies at NTNU. The current implementation is based on some inadequate documentation from the 2009 implementation. The 2009 implementation was in use up to 2014 and was notorious for blowing output transistors. As well as for being put together with hot glue. In 2014 an effort was begun to improve the reliability and portability of the tesla coil. A new implementation was created with the design split into modules to ease the further development. The connectors and the casing for the driver was replaced improving portability greatly. The coil rig was also replaced as it had the tendency to catch fire. This implementation still has some problems as outlined and attempted corrected in this report.

Thanks should be made to Omega Verksted who has financed the parts used for this project.

# Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
1.1	Tesla . . . . .	1
1.2	DRSSTC . . . . .	2
1.2.1	Triggering signal . . . . .	4
1.2.2	Timing diagrams . . . . .	4
1.3	Reliability . . . . .	7
1.3.1	Fault tree . . . . .	7
1.3.2	Maintainability . . . . .	7
1.4	Mass producability . . . . .	8
1.5	Customer . . . . .	9
<b>2</b>	<b>System Architecture</b>	<b>9</b>
2.1	Card inserted bus . . . . .	10
2.2	Optical channel . . . . .	11
2.2.1	Carrier wave . . . . .	11
2.2.2	Modulation . . . . .	12
2.3	Bus . . . . .	12
<b>3</b>	<b>Schematics</b>	<b>14</b>
3.1	Altium designer . . . . .	14
<b>4</b>	<b>Layout</b>	<b>15</b>
4.1	PCB identification . . . . .	15
4.2	Power back plane (TK530) . . . . .	15
4.3	Signal back plane . . . . .	16
4.3.1	Signal module form factor . . . . .	16
4.3.2	Power supply module form factor . . . . .	17
4.3.3	Power module form factor . . . . .	17
<b>5</b>	<b>Results</b>	<b>17</b>
<b>6</b>	<b>Conclusion</b>	<b>19</b>
<b>7</b>	<b>Further work</b>	<b>19</b>
<b>Appendices</b>		<b>21</b>
<b>A</b>	<b>Specification</b>	<b>21</b>
A.1	TK100 Signal generator . . . . .	21
A.2	TK500 Driver . . . . .	22

A.3	TK1000 Spolerigg . . . . .	25
<b>B</b>	<b>Schematics</b>	<b>26</b>
<b>C</b>	<b>Layout</b>	<b>43</b>
C.1	TK510 . . . . .	44
C.2	TK511 . . . . .	48
C.3	TK520 . . . . .	50
C.4	TK530 . . . . .	52
C.5	TK531 . . . . .	56
C.6	TK532 . . . . .	58

## List of Figures

1	A tesla coil in use . . . . .	2
2	Block diagram . . . . .	2
3	Transformation of $X_1$ to two level [5] . . . . .	3
4	Measurements of signals. . . . .	5
5	Different tones . . . . .	5
6	Different volumes . . . . .	5
7	One pulse on $X_1$ . . . . .	6
8	One pulse on $X_1$ , longer input pulse . . . . .	6
9	One pulse on $X_1$ , longer on time . . . . .	6
10	Multiple pulses on $X_1$ (max on: 2, min between: 12) . . . . .	6
11	Multiple pulses on $X_1$ (max on: 2, min between: 12) . . . . .	6
12	Multiple pulses on $X_1$ (max on: 2, min between: 12) . . . . .	6
13	Fault tree for destructive failure of DRSSTC . . . . .	9
14	Fault tree for non-destructive failure of DRSSTC . . . . .	9
15	Block diagram . . . . .	10
16	Bus interface . . . . .	11
17	Diagram of optical channel . . . . .	12
18	Modulated signal timing diagram . . . . .	12
19	Signal module card slot connector (detail from schematic of TK510 Signalbakplan (slot 0)) . . . . .	14
20	Detail from TK530 PCB . . . . .	15
21	Signal module pcb . . . . .	16
22	Power module form factor . . . . .	17
23	Fault tree for destructive failure of DRSSTC . . . . .	18
24	Fault tree for non-destructive failure of DRSSTC . . . . .	18

26	Signal module card slot connector (detail from schematic of TK510 Signalbakplan) . . . . .	23
----	---	----

## List of Tables

1	Failure sources . . . . .	8
2	Backplane signals. . . . .	13



## 1 Introduction

Universities, knowledge centers and other institutions has the need for equipment that demonstrates physical phenomena in interesting and audience friendly ways. An example of this is a Double Resonant Solid State Tesla Coil (DRSSTC). This is a contraption that by the use of high voltage generates a sequence of electrical discharges. When these discharges happen in air a sound wave is generated. By modulating the frequencies of these discharges one can generate sound with different tones. A DRSSTC can in this way be made into a musical instrument. For demonstration purposes it is important to control both streamer length and tone quality on such an musical instrument. It is further desirable that the instrument is portable, reliable, and safe to use. In a portable DRSSTC consisting of several modules it is desirable to quickly detect if errors occurs, i.e. in the context of transport. With the base in an existing circuit design it should be designed a robust implementation with possibility to detect errors. It is further desirable to develop a rough understanding of how different design parameters affects the performance of an DRSSTC.

The system should take audio as input and output acoustic audio by means of an high voltage electric discharge in air creating plasma (streamer) by the means of a resonant transformer (tesla coil). The system should also be designed such that it will always be functional, and in the case of the system not being functional should fail in a safe and non-destructive way (safe having priority over non-destructive). As well as indicating which part of the system is non-functional. The system should also be designed in such a way that this non-functioning part may be swapped for a spare functioning part.

Figure 1 shows a DRSSTC in use where a streamer has formed from the top load to a grounded copper object.

### 1.1 Tesla

The Tesla Coil is a form of resonant transformer invented by Nikolai Tesla and used for experiments with artificial illumination [9]. A resonant transformer consists of two inductively coupled coils, each loaded with a capacitance such that they get the same resonance frequencies. The resonant transformer has since gotten a lot of applications, among others; RFID, NFC, and Wireless charging. The resonant transformer in the form of the Tesla Coil has also become a popular entertainment device.



Figure 1: A tesla coil in use  
Foto: Sindre Vaskinn Hunn

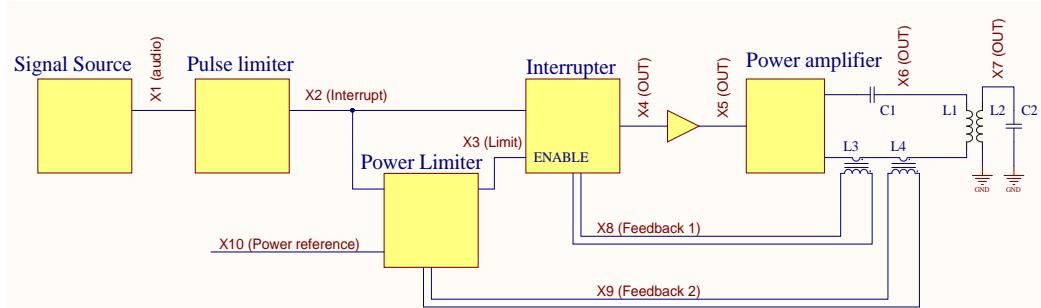
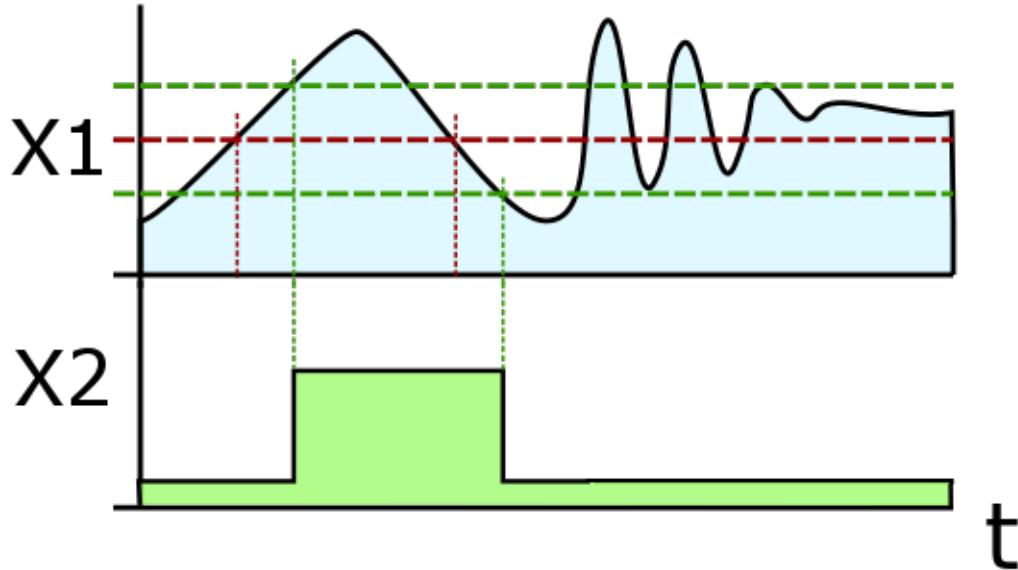


Figure 2: Block diagram

## 1.2 DRSSTC

DRSSTC is an acronym for Dual Resonant Solid State Tesla Coil. Dual resonant means that we have two resonant circuits inductively coupled, and tuned to the same resonance frequency. Solid state means that we drive these resonant circuits actively with transistors. The origins of the DRSSTC is not well documented but it is commonly accepted that it was conceived on "The tesla coil mailing list" [2].

The signal pathway consists of a signal source, pulse limiter, power limiter, interrupter, amplifier, and power amplifier see fig. 2. The signal source provides the signal to be output on the coil, often the signal source is a

Figure 3: Transformation of  $X_1$  to two level [5]

musical recording. The input signal should be monophonic, arpeggio<sup>1</sup> may be used. The input signal may be two level.

First the input signal  $X_1$  goes into the pulse shaper, which transforms the signal to two, level limits on-time of each pulse, and enforces a minimum time between pulses. In fig. 3 an example  $X_1$  is shown and a corresponding  $X_2$ , here we see that the transformation to two level is done with a schmitd trigger, and that the pulses following immediately after the first pulse is suppressed. (section 1.2.2). Then the signal  $X_2$  is connected to the interrupter which on a positive flank outputs a positive flank  $X_4$ , which is amplified  $X_5$  and  $X_6$  and sent into the resonant circuit ( $C_1$ , and  $L_1$ ). This triggers the step response of the resonant circuit. Then a positive feedback loop  $X_8$  drives  $X_4$  at the resonant frequency of the resonant circuit (the resonant frequency is in the order  $f_0 = 100\text{kHz}$ ). This is achieved by inverting the output when the current through  $C_1$  and  $L_1$  passes through zero (as measured through  $L_3$ ). This continues until either the input pulse  $X_2$  goes low or the limit signal from the limiter  $X_3$  goes low. The limiter also measures the current flowing through  $C_1$  and  $L_1$ , but this signal  $X_9$  is rectified and fed through a low pass filter before being compared to a preset level  $X_{10}$ . This comparison measures the power dissipated in the resonant circuit. If the power exceeds the preset level the enable signal  $X_3$  is set low

<sup>1</sup>The sounding of the notes of a chord in rapid succession instead of simultaneously.

until the next rising edge of the input signal  $X_2$ .  $X_{10}$  is set by a multi turn potentiometer.

The resonant circuitry consists of  $C_1$ ,  $L_1$ ,  $C_2$  and  $L_2$ , where  $L_2$  is magnetically coupled with  $L_1$  with a degree of approximately 0.2.  $C_1$  is a bank of capacitors with high voltage and current rating and low equivalent series resistance (ESR).  $L_1$  is an inductor with high cross section area and few turns (in the magnitude of 5 turns).  $L_2$  is an inductor with low cross section area and a high number of turns (in the magnitude of 4000 turns).  $C_2$  consists of a sphere or toroid for one plate, and the grounded (safety ground) surroundings. Ground is connected through the safety ground in the electrical socket used to power the DRSSTC.  $L_3$  and  $L_4$  are current sensing transformers.

Figure fig. 4 shows a measurement of these signals. Channel 2 (Green) shows the feedback signal  $X_8$  after it is fed through a protection network limiting the voltage (See the schematic for TK514 in appendix B). Channel 4 (Red) shows an internal signal  $Y_1 = X_2 \&& \bar{X}_3$  in the interrupter. This as long as this signal is high the output signal  $X_4$  will swing at the resonant frequency. Note that we would expect  $X_8$  to be zero as long as channel 4 is low, but there is some delay before the resonant circuit stops swinging after the supply of energy stops. Also note the interference on  $X_3$  and  $Y_1$  from the output signal  $X_6$ .

### 1.2.1 Triggering signal

The triggering signal  $X_2$  is two level and contains two pieces of information from  $X_1$ , the frequency  $f$  (tone) and the volume (intensity). The frequency is given by the time  $T$  between the positive flanks of the signal  $f = \frac{1}{T}$ . This is the base harmonic of the acoustic tone heard at the output of the system. The volume is given by the duty cycle of the pulses (the relationship between the pulse being high and the total period  $T$  of the pulse. Figure 5 shows different tones, and fig. 6 shows different volumes.

### 1.2.2 Timing diagrams

fig. 7 to fig. 12 shows different examples of input pulses, and corresponding output pulses. Note that the timings and frequencies are not to scale, only relative timings.

Figure 7 shows a single pulse on the input signal  $X_1$ , here we see  $X_2$  is limited to a certain width. We also see that  $X_4$  and  $X_8$  goes high when  $X_2$  goes high, oscillates at the resonance frequency of the resonance circuit, and goes low when  $X_2$  goes low. Figure 8 shows the same principle, only with a



Figure 4: Measurements of signals.  
Channel 1 (Yellow):  $X_2$ , 2 (Green):  $X_8$ , 3 (Blue):  $X_3$ , 4 (Red):  $X_2 \& \bar{X}_3$ . Voltage axis: 5V/div. Time axis: 200 $\mu$ s/div.



Figure 5: Different tones

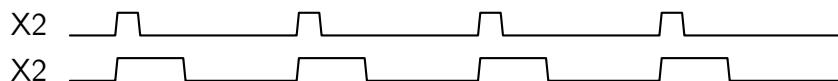


Figure 6: Different volumes

longer pulse on  $X_1$ .

Figure 9 shows the same input signal as fig. 8 but with a different setting of the on-time on the pulse limiter (allowing longer on-time).

Figure 10 to fig. 12 shows multiple pulses on  $X_1$  and corresponding signals on  $X_2$ . With on-time set to 2 units and minimum time between pulses set to 12 units.

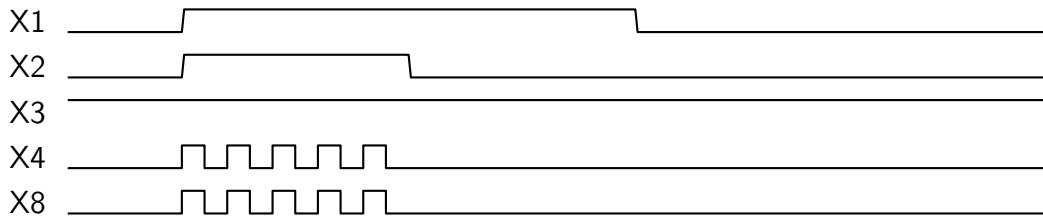


Figure 7: One pulse on X1

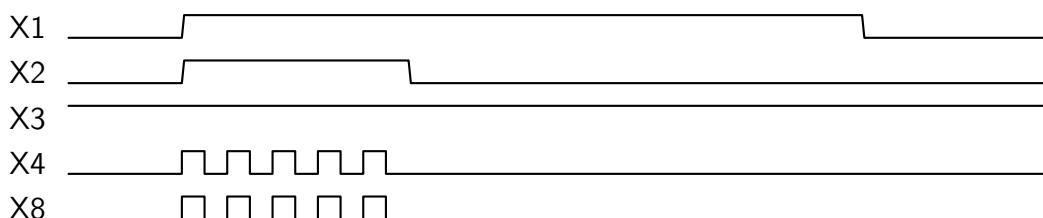


Figure 8: One pulse on X1, longer input pulse

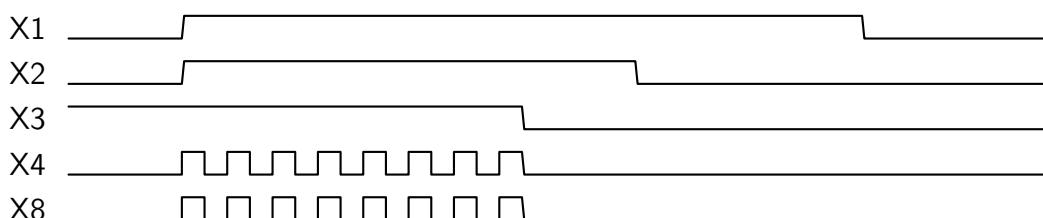


Figure 9: One pulse on X1, longer on time

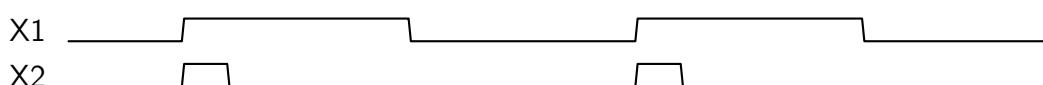


Figure 10: Multiple pulses on X1 (max on: 2, min between: 12)

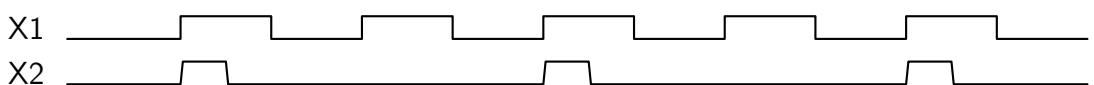


Figure 11: Multiple pulses on X1 (max on: 2, min between: 12)

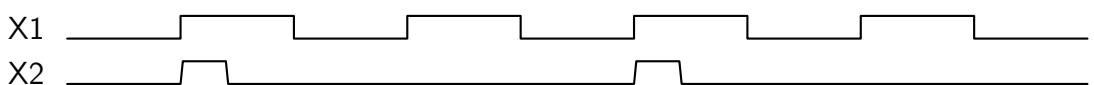


Figure 12: Multiple pulses on X1 (max on: 2, min between: 12)

## 1.3 Reliability

In every system there is certain demands for reliability (reliability describes the ability of a system to function under certain conditions for a specified period of time). The DRSSTC should function in indoor conditions and dry outdoors weather, the DRSSTC should also function after sitting in storage for up to one year. And should function after transportation by trolley and or car. And after sitting on a stage during rigging. The DRSSTC should function for several years with transportation and rigging up to 30 times a year.

To achieve this the system should also have high maintainability. It should take a maximum of one day to fix an error.

### 1.3.1 Fault tree

A method for analyzing reliability of a system is using a fault tree [3]. The fault trees for this system is shown in fig. 13 and fig. 14. The inputs are failure sources that can occur these are listed in table 1. The probability  $P$  for each failure source is calculated from the number of times this failure has occurred divided by the number times the system has been used. These numbers are extracted from the log entries in Omega Verksteds log book for their tesla coil [11]. A total of 33 uses are logged in the period 2013-08-22 to 2016-11-07, the real number of uses should be assumed higher as the log book is not written at each use due to human error. The fault sources that does not occur in the log book is assumed to have a probability  $P$  of less than 0,03. Some of these failure sources are due to operator error and is outside of this report to fix. These failures sources are F3, F5, and F7 they are attempted to fix with procedures [12]. The failure source with the highest probability  $P = 0,12$  is F8 this is a failure that does not occur by itself but as a consequence of other failure sources as shown in fig. 13 and must thus be fixed by addressing the failure sources leading to this failure. The failure source remaining with the highest probability  $P = 0,09$  is F2 defective optical cable. By using the standard rules of combining probabilities with logic functions we get a calculated probability of failure of  $P(F) = 0,71$ . The probability for destructive failure  $P(F_8)$  used in calculating the probability for failure  $P(F)$  is the value gotten from calculating the output from the destructive failure fault tree  $P(F_8) = 0,666$ , and not the value listed in table 1.

### 1.3.2 Maintainability

The goal of errors taking a maximum of one day to fix is set so that you will always have a functioning system by testing it one day before it is to be used

	P	Description
F0	0,03	System is transported and vibrations shakes loose the wires on the high voltage side of the system.
F1	<0,03	No carrier wave (CW) detection is implemented in the optical receiver of the driver TK500, or this detection is defective.
F2	0,09	Optical cable is defective (someone has stepped on it).
F3	0,03	Optical cable is missing.
F4	< 0,03	Pulse shaper (TK100) is defective.
F5	0,06	Pulse shaper is set to too high volume.
F6	0,03	Power limiter is defective.
F7	0,06	Power limiter is set to too high power.
F8	0,12	Destructive failure happens, power amplifier or the load capacitor C1 catches fire.
F9	0,03	Internal cables are disconnected due to vibrations while transporting the system.

Table 1: Failure sources

for a performance. By partitioning the system into modules with limited components, the assembly time for one module is kept short. By keeping spare modules, and spare components. You will be able to either just switch the module, which by the use of a backplane takes only a matter of minutes. Or assemble a new module which should take less than one day.

## 1.4 Mass producability

To be able to mass produce the system some care needs to be taken during the design process.

When drawing the schematics each component has a link to a database with ordering information, price, and number and location in local warehouse.

Altium designer contains tools for automatic bill of materials (BOM) generation. This can be tailored to ones supplier, such that the output file can be uploaded to the supplier to order the components needed for manufacturing the design.

Components needs to be placed, and footprints drawn according to IPC7351(A,B, or C) to be able to manufacture the design at a factory.

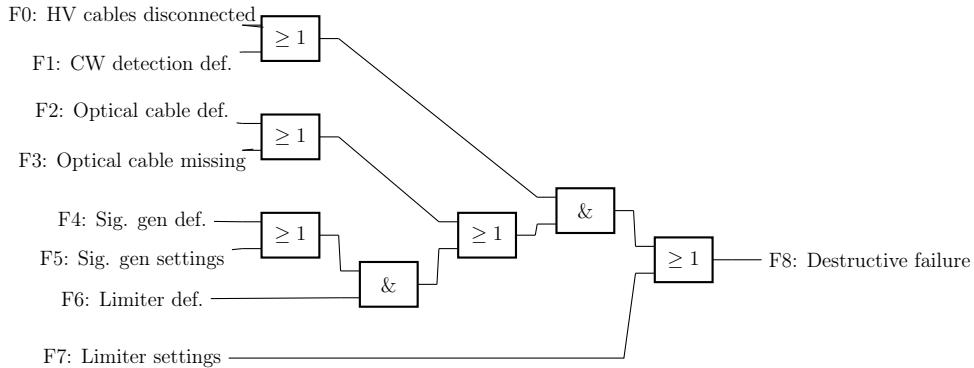


Figure 13: Fault tree for destructive failure of DRSSTC

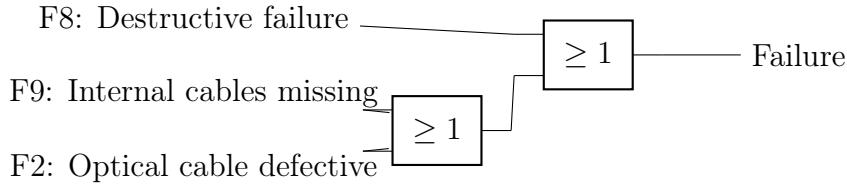


Figure 14: Fault tree for non-destructive failure of DRSSTC

## 1.5 Customer

The customers of the system is Omega Verksted<sup>2</sup>, research projects, and amusement parks. These customers can be divided into two groups, customers who will be moving the DRSSTC and packing it down when not in use, and customers who will have it in a permanent installation. We will focus on the customers moving the DRSSTC around since this will put the toughest requirements on the design.

## 2 System Architecture

To achieve the goal of high maintainability a back plane architecture was chosen. The choice of back plane is also defended as a way to eliminate wires and connectors between different pcbs, as wires can fall out during transport, and glue is not an alternative as it should be easy to change a module. The back plane provides a good electrical and mechanical connection as well as some additional features (card detection). The back plane is split in two, one signal back plane and one power back plane. On the signal back plane

<sup>2</sup>Omega Verksted is a association of electronics and hobby interested students at the Norwegian University of Science and Technology (NTNU) founded in 1971.

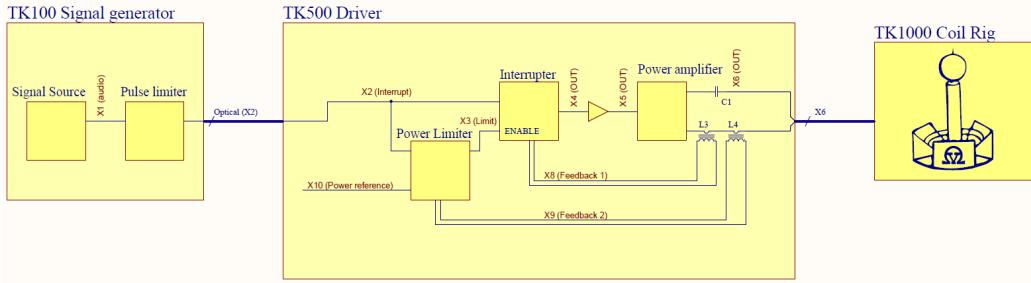


Figure 15: Block diagram

there is six module slots plus three power supply slots. On the power back plane there are two power amplifier slots (the power amplifier is split into two identical circuits), and one slot for the load capacitor.

The signal source needs to be a long distance away from the coil rig due to safety reasons, and the power amplifier needs to be as close to the coil rig as possible to keep ohmic losses in the resonant circuit as low as possible. The Interrupter and power limiter has low voltage feedback signals X8 and X9 as inputs. Because of the nature of a tesla coil, there is a lot of electromagnetic interference (EMI) present such that low voltage signals needs to be sent through a channel that is robust against electromagnetical noise. Thus the system is partitioned such that the signal source and pulse shaper TK100 is placed together, and the rest of the system placed together in a shielded enclosure TK500. The signal from the pulse shaper X2 should then be sent through a robust channel. Optical plastic fibre is chosen described in section 2.2. X8 and X9 are then short and inside a shielded enclosure, and no other protection from EMI is required.

Inside TK500 we have both high power and low power signals. These should be separated such that the high power signals does not provide interference for the low power signals. And so that the electronics with low power signals can be designed with lower voltage and power requirements. This is solved by creating a signal back plane TK510 and a power back plane TK530, connected via an galvanic isolation TK520.

In addition some user interface is needed on the driver TK500. This is partitioned into a sub system called TK540.

## 2.1 Card inserted bus

When partitioning the system into several modules physically spread over multiple pcbs there is a risk of one module not being connected to the system, either because of issues with transportation, or by human error.

To mitigate this risk, detection of which cards is inserted into the back plane is implemented. This is done by a bus. The bus consists of one wire named Card\_inserted, pulled high by a  $10k\Omega$  resistor, fig. 16 shows how each card slot interfaces to the card inserted bus, S1D shorted when a card is inserted and Card\_inserted is the bus. When no card is inserted into the slot the gate of the nmos is pulled high by R1 and the nmos goes into the triode region and pulls the bus low. When a card is inserted it pulls the gate low. And the nmos goes into cut-off. This circuit is replicated at each card slot.

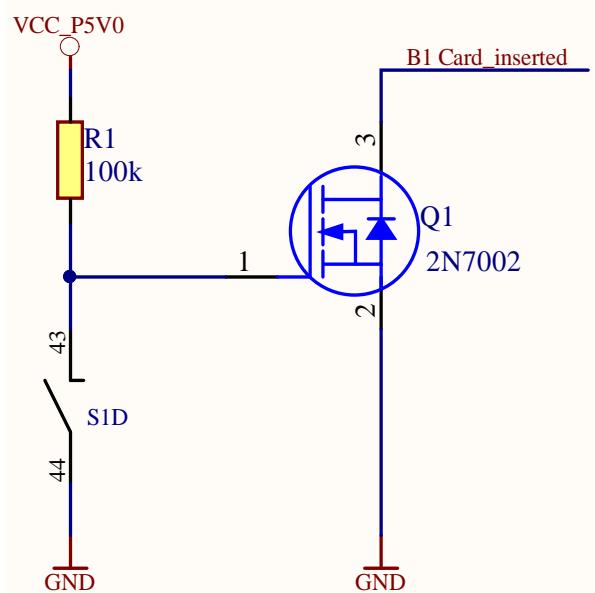


Figure 16: Bus interface

## 2.2 Optical channel

As mentioned in section 2 a robust channel is needed for signal X2. For this plastic optical fibre is chosen. To further increase the robustness the signal (X2) should be modulated. To reduce complexity a simple modulation should be chosen. To remove the failure source of the optical cable missing (F3) and possibly some cases of defective optical cable (F2) the carrier wave (CW) should be chosen so that it is easily detectable in the receiving end.

### 2.2.1 Carrier wave

The carrier wave CW for the optical channel is a square wave, and should have a sufficiently high frequency  $f = \frac{1}{T}$  to transfer the triggering signal X2,

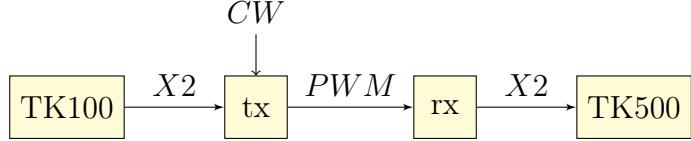


Figure 17: Diagram of optical channel

in addition to be easily detected in the receiving end. X2 contains two parts of information the frequency and the volume. The period  $T$  should be shorter than the lowest desirable positive pulse on X2  $T_{X2min} = 4\mu s$ .  $f_{CW} > \frac{1}{T_{X2min}}$  The shortest desirable pulse on X2 is a length that allows turning the volume down without a noticeable step before shutoff. This length is taken from the previous implementation of this system.

### 2.2.2 Modulation

The triggering signal should be pulse width modulated PWM with a logical high having a duty cycle of 80% and logical low having a duty cycle of 20%.

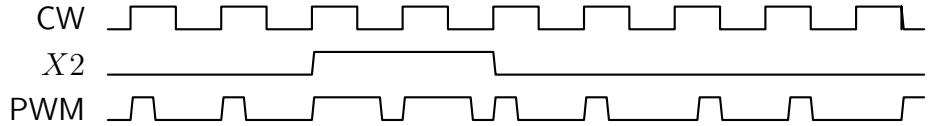


Figure 18: Modulated signal timing diagram

## 2.3 Bus

A set of signals should be available to all card slots on the signal back plane these signals are signals  $B1$  to  $B14$  in table 2. The reason these signals should be present on all connectors is so that any module can be inserted in any slot of the back plane. In addition some unique signals should be present on each connector these are the other signals in table 2. Signals  $n\_KI$ ,  $n\_FE$ ,  $n\_ST$ , and  $n\_INT$  are signals which should drive LEDs on the front panel to indicate status of the module to the operator. The signal  $n\_KNP$  should be connected to a button on the front panel for each card module slot on the signal back plane, for the operator to give simple feedback to the module. ' $n$ ' is an integer from 0 to  $N$  denoting the id of the module slot. The signals  $FP\_1$  to  $FP\_5$  are signals to the front panel reserved for future use. The signals  $AUX1\_A$  &  $AUX1\_B$  and  $AUX2\_A$  &  $AUX2\_B$  are connectors used for the signals  $X5$ ,  $X8$ ,  $X9$ ,  $X10$  and the PWM signal from the optical

channel, and added to all slots so that any module can be inserted into any slot, given that the aux connections are connected at the correct slot. The pinout of the connector is shown in fig. 19

	Signal name	Description
B1	Card_inserted	The card inserted bus described in section 2.1
B2	Trigger	The triggering signal $X_2$
B3	Limit	The output from the power limiter $X_3$
B4	Interrupt	The output from the interrupter $X_4$
B5 to B14	N.A.	Reserved for future use
A1	n_KI	Card inserted (low when card is inserted floating otherwise as described in section 2.1)
A2	n_FE	Active when fault detection of module detects a fault
A3	n_ST	A status signal from the module
A4	n_INT	Interrupt signal from the module, low when the module accepts the system firing, high otherwise.
A5	n_KNP	Button input to the module from the front panel
A6 to A10	FP_1 to FP_5	Signals to the front panel reserved for future use
A11	AUX1_A	'A' branch of, Auxillary input/output to the module terminated in a connector close to the card slot connector.
A12	AUX1_B	'B' - branch of AUX1
A13	AUX2_A	Same as AUX1
A14	AUX2_B	Same as AUX1

Table 2: Backplane signals.  
'n' is the id of the connector slot

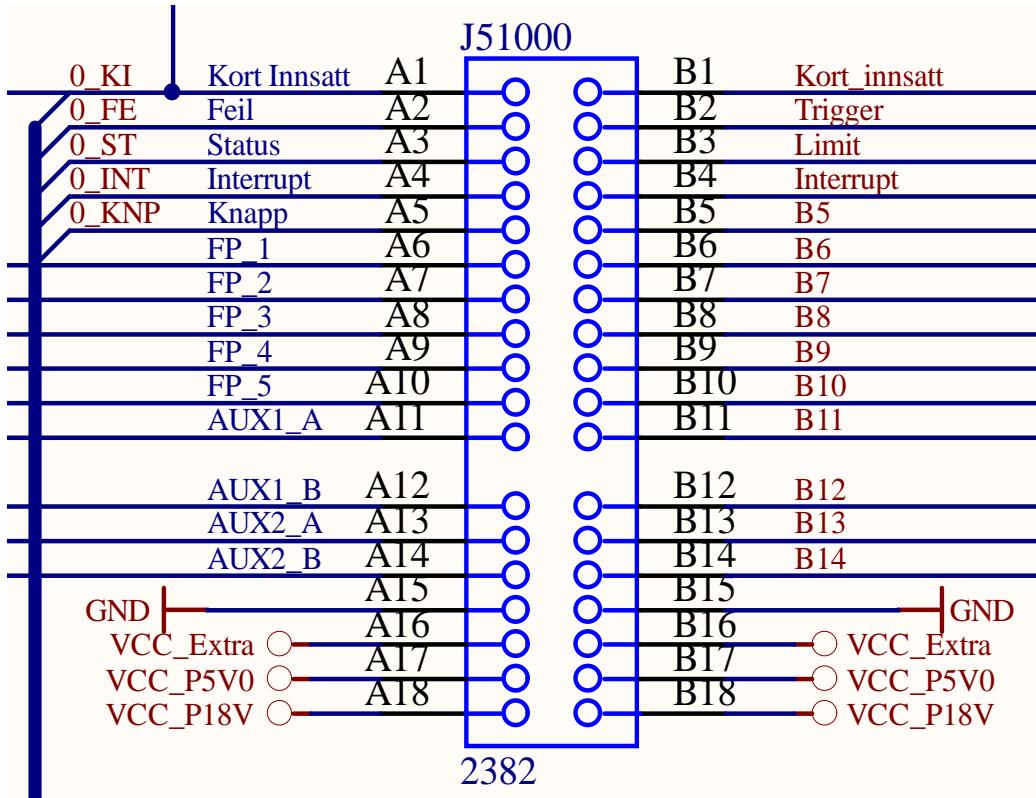


Figure 19: Signal module card slot connector (detail from schematic of TK510 Signalbakplan (slot 0))

### 3 Schematics

The schematics for this system is drawn in Altium designer and is attached in appendix B. Note that appendix B is best printed on A3 paper. All digital produced material have been stored in a central Git-based version control system which is accessible at [13]. The schematics is found under '05\_HardwareTK500\_DriverProjectOutputsTK500\_design\_documentation.PDF' Also note that not all of the schematics are finished, and that the schematics are in norwegian.

#### 3.1 Altium designer

Altium Designer [1] is a powerful CAD tool for designing printed circuit boards (PCB). This type of tool allows the designer to first design or import each component one by one into the program, that also is used in the full design. When this is finished, the the schematics can be drawn and synced

with a layout tool.

Alternatives to Altium Designer is Eagle [10], kicad [7], Proteus [4], ultiboard [6] and orcad [8]. The reasons for Altium designer to be chosen over the others is Eagle, and kicad (where kicad is considered an open source version of Eagle) is that Eagle has very few automations, thus you end up spending a lot more time to do the same work. The rest of the programs were not chosen of more subjective reasons. In addition to these reasons these CAD programs are very expensive so a key point in choosing Altium Designer is that NTNU has a licence for students. Also we have previous experience using Altium Designer, both from hobby work and relevant summer internships.

## 4 Layout

The layout for this system is also done in Altium desginer and is attached in appendix C. The layout for TK510, TK511, TK520, TK530, TK531, and TK532 is completed, and attached. The source files in Altium format can be found at [13].

### 4.1 PCB identification

To easily identify the pcbs (and modules) markings are placed in silk screen of all the pcbs in the same way. The Part number of the module, the date manufactured. And Omega Verksteds logo. See fig. 20.

### 4.2 Power back plane (TK530)

The stackup for the power back plane is two layers with no copper plane fill. Two layers is chosen because of the low complexity of the layout, and no copper plane fill is chosen to increase separation of low and high voltage signals. The traces for the HVDC supply voltage are drawn as thick as reasonable and the supply connections are placed in the middle between the two power amplifier modules. The connections for the output signal are



Figure 20: Detail from TK530 PCB

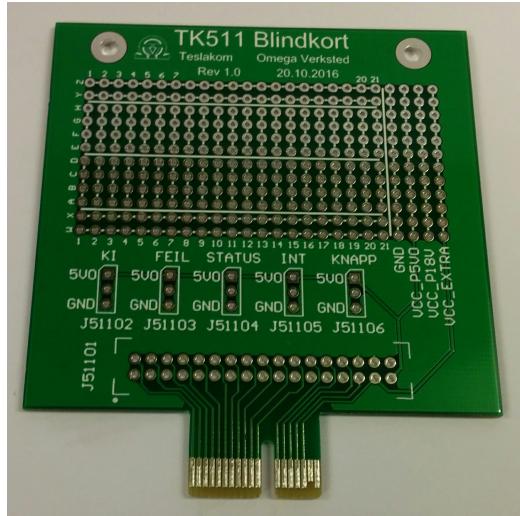


Figure 21: Signal module pcb

placed as close to the card connectors as possible, and the solder mask on the trace from the power amplifier and the load capacitor is omitted so that additional solder may be added to the trace to increase the area of the trace. Warning labels are added next to all exposed metal with higher than 50V (peak) voltage. The width of the pcb is chosen from the price breaks of the pcb supplier. Card holders to add mechanical stability to the inserted modules are mounted directly to the pcb, these guide the modules and ensures the module mates correctly with the connector. Some mechanical fastening to the chassis should also be used to fix the module in place. The thickness of the substrate was chosen to be 3mm to increase the mechanical strength.

### 4.3 Signal back plane

The connectors for the power modules are offset to prevent power modules to be inserted in signal module slots and vice versa. The same card holders as used on the power back plane are used on the signal back plane. The width of the signal back plane is chosen from the price breaks of the pcb supplier.

#### 4.3.1 Signal module form factor

The width of the signal module is given by the width of the signal back plane minus the space used for the card holders. The height is chosen from the height of the card holders, and the closest price break of the pcb supplier. The form factor chosen is shown in fig. 21



Figure 22: Power module form factor

#### 4.3.2 Power supply module form factor

The form factor for the power supply modules is the same as for the signal modules with the exception of the connector being offset.

#### 4.3.3 Power module form factor

For the power modules back plane connectors from samtec with four powerful pins and 16 signal pins was chosen. The width is chosen as the same as the signal modules. The form facor chosen is shown in fig. 22.

## 5 Results

Before any improvements the system had a probability of failure  $P(F)=0,71$ . After improvements we have removed F0 and F9 from the general fault tree, and F2, F3 from the destructive fault tree (F8) and the calculated probability of failure is reduced to  $P(F)=0,18$ . The updated fault trees are shown in fig. 23 and fig. 24. The calculated probability for destructive failure  $P(F8)$  is reduced from 0,67 to 0,10.

In fig. 25a the power amplifier with and without back plane is shown

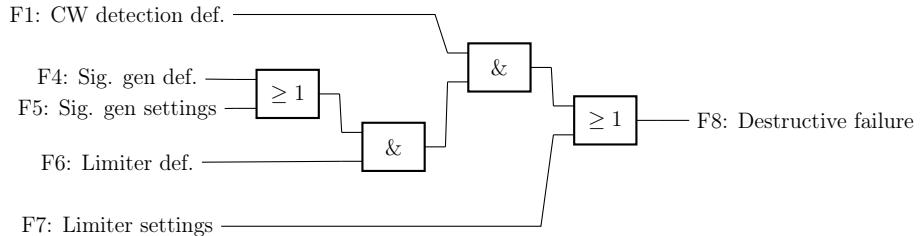


Figure 23: Fault tree for destructive failure of DRSSTC


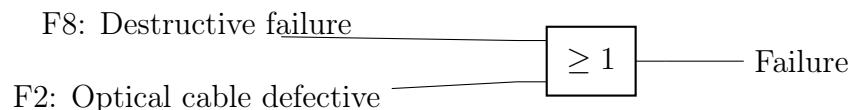


Figure 24: Fault tree for non-destructive failure of DRSSTC

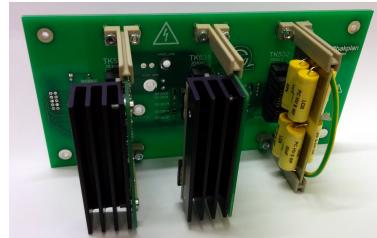

(a) Power amplifier without back plane



(b) Power amplifier with back plane

## 6 Conclusion

The existing circuit design and implementation had problems with reliability as described in section 1.3. The reliability of the system was calculated by the use of a source tree based on logged faults to  $P(F)=0,71$ . After implementing a back plane design, and adding carrier wave detection on the input signal the calculated reliability increased to  $P(F)=0,18$ . This is a large increase in reliability. Portability was present in the existing implementation, and has been increased by removing failure sources that occurred when moving the system.

## 7 Further work

The next step in increasing reliability in the system is adding more complex fault detection on each module, and exploiting the status signals made available. The next step in improving the DRSSTC is looking at how different design parameters affects the performance with relation to streamer length and tone quality.

## References

- [1] Altium. Altium home page. <http://www.altium.com/>, 2015. [Online; accessed 2015-04-08].
- [2] Chip Atkinson. Tesla coil mailing list. <http://www.pupman.com/>, 2016. [Online; accessed 2016-11-17].
- [3] R.E. Barlow. *Fault Tree Analysis. Encyclopedia of Statistical Sciences*. 4. 2006.
- [4] Labcenter electronics. Labcenter electronics. <http://www.labcenter.com/index.cfm>, 2015. [Online; accessed 2015-04-08].
- [5] FDominec. Tesla coil mailing list. [https://commons.wikimedia.org/wiki/File:Smitt\\_hysteresis\\_graph.svg](https://commons.wikimedia.org/wiki/File:Smitt_hysteresis_graph.svg), 2007. [Online; accessed 2016-12-15].
- [6] National instruments. National instruments ultiboard. <http://www.ni.com/ultiboard/>, 2015. [Online; accessed 2015-04-08].
- [7] KICAD-pcb. Kicad-pcb. <http://www.kicad-pcb.org/>, 2015. [Online; accessed 2015-04-08].
- [8] OrCAD. Orcad. <http://www.orcad.com/>, 2015. [Online; accessed 2015-04-08].
- [9] N. Tesla. Experiments with alternate currents of very high frequency and their application to methods of artificial illumination. *Transactions of the American Institute of Electrical Engineers*, VIII(1):266–319, Jan 1891.
- [10] Cadsoft USA. Cadsoft usa. <http://www.cadsoftusa.com/>, 2015. [Online; accessed 2015-04-08].
- [11] Omega Verksted. *Loggbok for teslacoil*. 2016.
- [12] Omega Verksted. *Prosedyrer for teslacoil*. 2016.
- [13] Øystein Smith et. al. Tesla-driver git repository. <https://github.com/Cable89/tesla-driver>, 2016. [Online; accessed 2016-12-17].

# Appendices

## A Specification

The system has been partitioned into sub-systems listed below. The sub systems has been assigned an arbitrary part number with the prefix "TK".

1. TK100 Signalgenerator
2. TK500 Driver
  - (a) TK501 Frontpanel
  - (b) TK502 Frontpanel LEDS
  - (c) TK510 Signalbakplan
  - (d) TK511 Blindkort
  - (e) TK512 Optisk Mottaker
  - (f) TK513 Limiter
  - (g) TK514 Interrupter
  - (h) TK516 Ekstra-PSU
  - (i) TK517 P5V0-PSU
  - (j) TK518 P18V-PSU
  - (k) TK519 Spenningsvakt
  - (l) TK520 GDT-Trafo
  - (m) TK530 Kraftbakplan
  - (n) TK531 Utgangstrinn
  - (o) TK532 Kondensatorkort
3. TK1000 Spolerigg

### A.1 TK100 Signal generator

The Signal generator Should take a wide range of inputs and output the triggering signal X2 for the driver. It consists of the pulse shaper and signal source mentioned in section 1.2 and shown in fig. 2. The output signal X2 should be sent through a optical plastic fibre to be against EMI as mentioned in section 2 and section 2.2. The output signal should also be modulated on a carrier wave as described closer in section 1.2.1 and section 2.2.1.

## A.2 TK500 Driver

The driver should take the output of the signal generator (TK100) as input, and output a 160VDC signal at the resonant frequency of the coil rig while the input signal is high and the peak power output does not exceed a configurable level. The driver should also have the capacitor of the primary resonant circuit integrated.

### **TK501 Frontpanel**

Should have a height of 4 standard rack units (4U) (17.78cm). Partitioned into multiple parts.

#### **Signal back plane card matrix**

Use the entire height, height divided into equal parts for each card in the signal back plane card. Each division should contain four LEDs; Green (Card inserted), Red (Fault), Green (status), Yellow (led in button). A field for card name. Space for buttons depending on the needs of the specific card.

#### **Power back plane card matrix**

Three leds for each of the three cards in the power back plane. Green (card inserted), Red (fault), Green (status).

#### **Display**

Voltage meter for output voltage. Ampere meter for output current.

#### **Power buttons**

Emergency stop Spring loaded rotary switch: slow start Momentary switch: Power on Momentary switch: Power off

## **TK510 Signalbakplan**

The signal back plane should have six slots for signal modules, and three slots for power supplies.

#### **Signal module slot**

The signal module slot should have the following signals:

- 1 bus with straps for pull up and pull down on bus lines. (B1-B14)

- Card inserted detection (A1)
- LED signals to front panel (A1-A5)
- Misc signals to front panel (A6-A10)
- Two contacts for signals other places inside chassis (A11-A14)
- Supply voltages and ground (A15-A18 & B15-B18)

The pinout on the module slot connector is shown in fig. 26

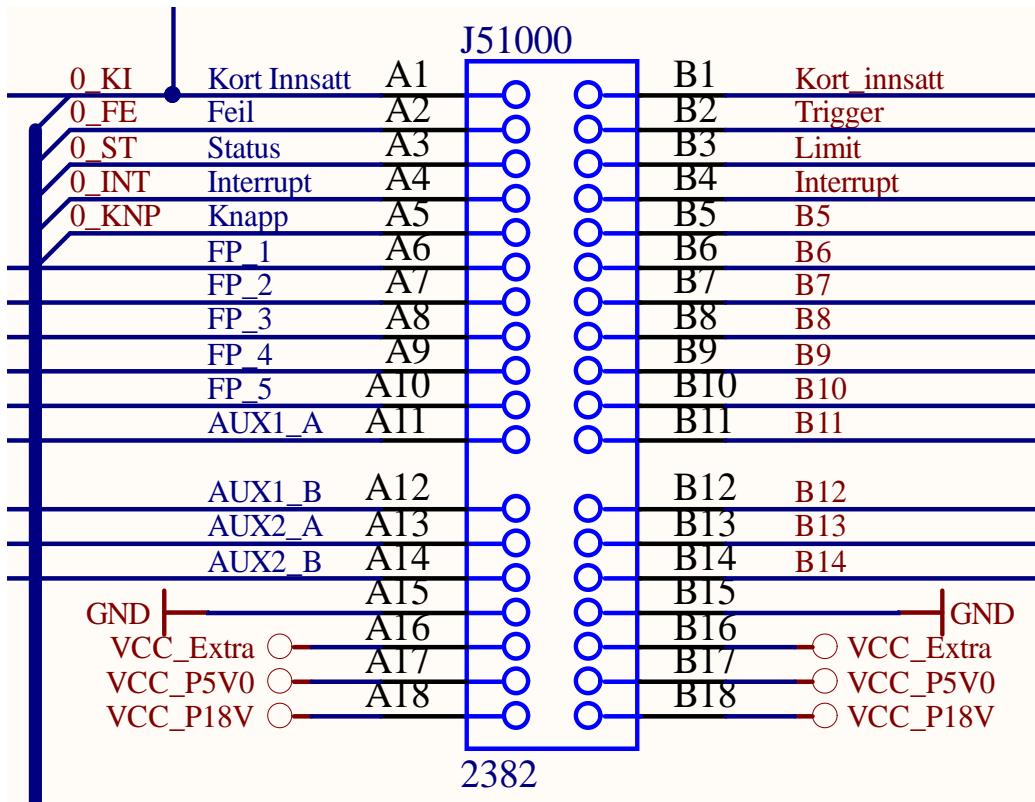


Figure 26: Signal module card slot connector (detail from schematic of TK510 Signalbakplan)

## TK511 Blindkort

The purpose of *TK511* is to take the space where no module is inserted into the signal back plane, and emulate an inserted module.

## TK512 Optisk Mottaker

The purpose of *TK512* is to convert the optical signal input into the driver *TK500* to an electrical signal, and a carrier wave detected signal.

## TK513 Limiter

The purpose of *TK513* is to prevent the coil rig *TK1000* from catching fire, and to keep the spark from turning yellow.

## TK514 Interrupter

The purpose of 514 is to fire the tesla coil when receiving input signal and to tune the output signal via a positive feedback loop to the systems resonance frequency.

## TK516 Ekstra-PSU

The purpose of *TK516* is to reserve a slot for future voltages.

## TK517 P5V0-PSU

The purpose of *TK516* is to provide 5V DC to the driver *TK500*.

## TK518 P18V-PSU

The purpose of *TK516* is to provide 18V DC to the driver *TK500*.

## TK519 Spenningsvakt

The purpose of *TK516* is to monitor the supply voltages in the driver *TK500*.

## TK520 GDT-Trafo

The purpose of *TK516* is to provide galvanic isolation between the signal back plane and the power back plane.

## TK530 Kraftbakplan

The purpose of *TK516* is to provide the connections and monitoring for the output stage *TK531* and the load capacitor *TK532*.

## **TK531 Utgangstrinn**

The purpose of *TK516* is to step up the voltage on the output.

## **TK532 Kondensatorkort**

The purpose of *TK516* is to provide the capacitance of the primary resonance circuit.

## **A.3 TK1000 Spolerigg**

The purpose of *TK516* is to look good and output the voltage arc or corona discharge.

## B Schematics

This page is intentionally left (almost) blank.

A

B

C


D

A

B

C


D

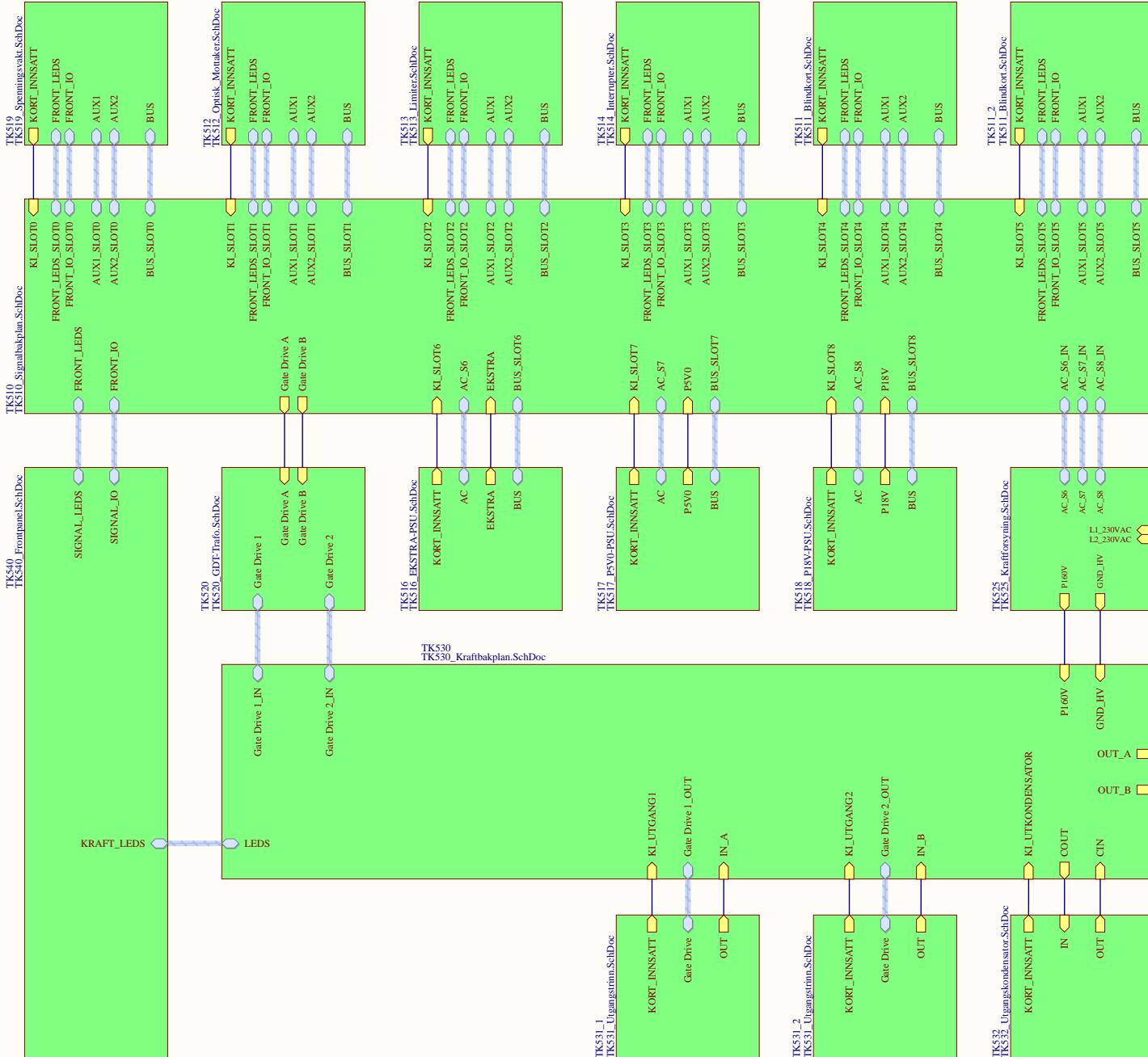

Title: TK500 Driver


Size: A3	Revision: 0	Author: Øystein Smith
Date: 26.04.2016	Sheet 1 of 20	Omega Verksted
File: D:\Temp\Tesla-Driver\05_Hardware\TK500_Driver\TK500_Driver.SchDoc		



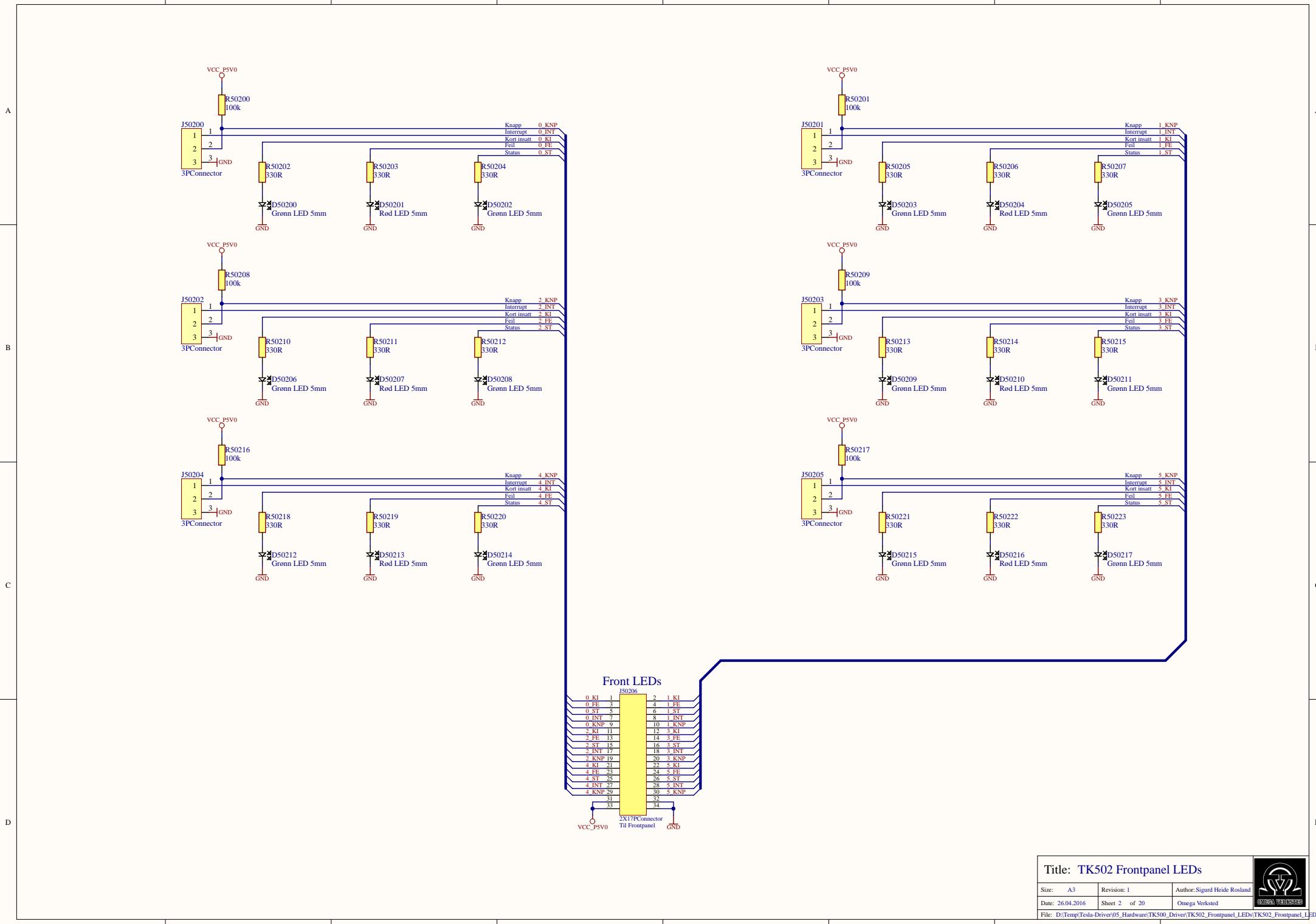

A

A

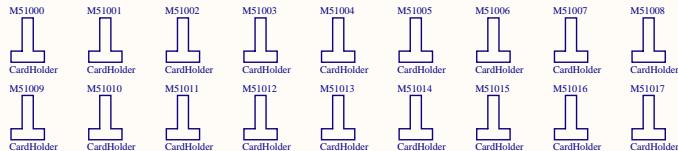

B

B

C

C


D

D

Title: TK510 Mekanisk



Size: A3	Revision: 0	Author: Øystein Smith
Date: 26.04.2016	Sheet 3 of 20	Omega Verksted
File: D:\Temp\Tesla-Driver\05_Hardware\TK500_Driver\TK510_Signalbakplan\TK510_Mekanisk.SchDoc		

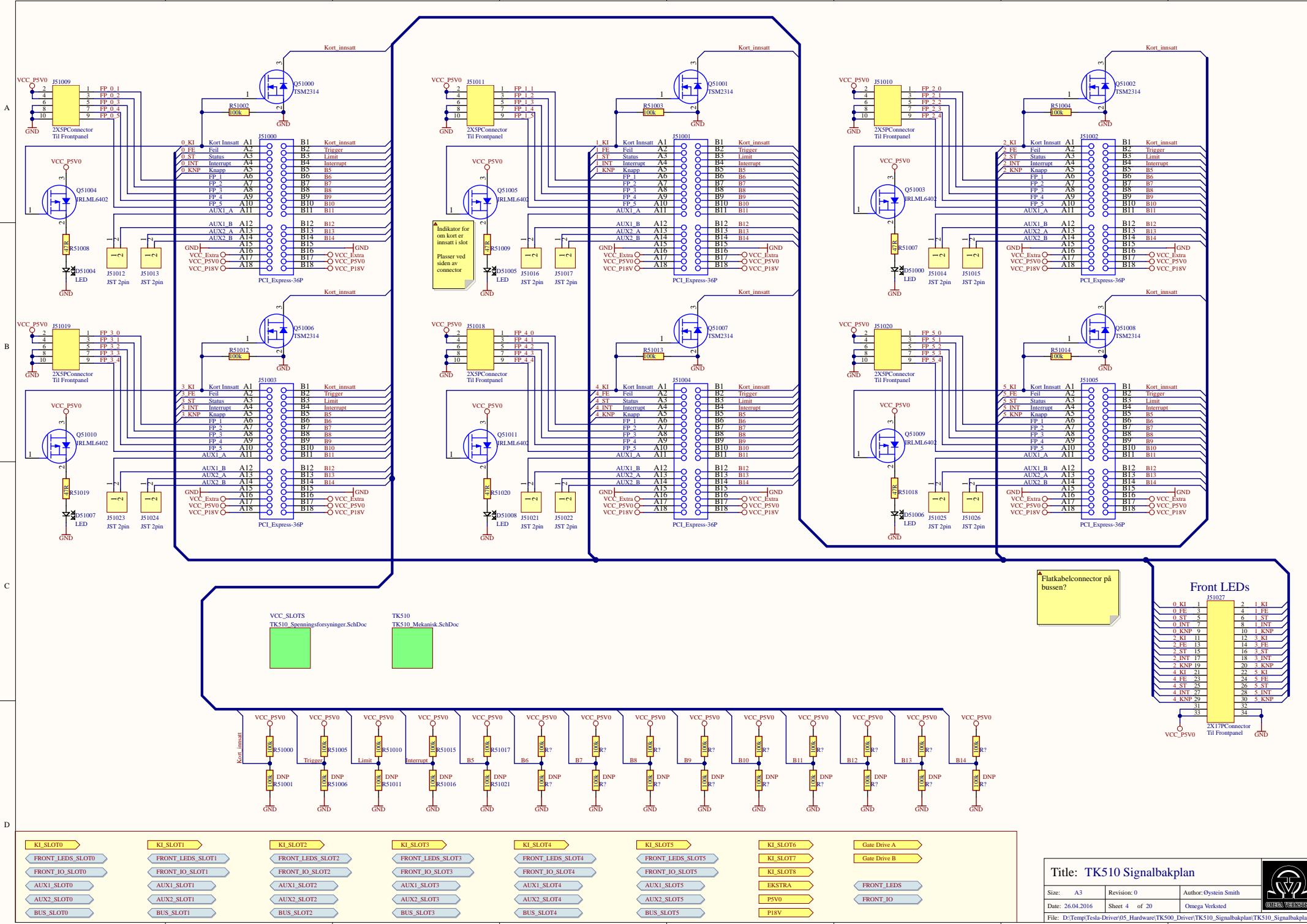

A

A

B


B

C

C

D

D

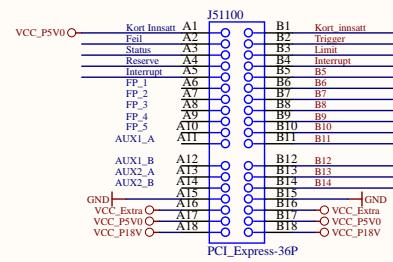

Title: TK511 Blindkort



Size: A3	Revision: 0	Author: Øystein Smith
Date: 26.04.2016	Sheet 5 of 20	Omega Verksted
File: D:\Temp\Tesla-Driver\05_Hardware\TK500_Driver\TK511_Blindkort\TK511_Blindkort.SchDoc		

A

A

B


B

C

C

D

D

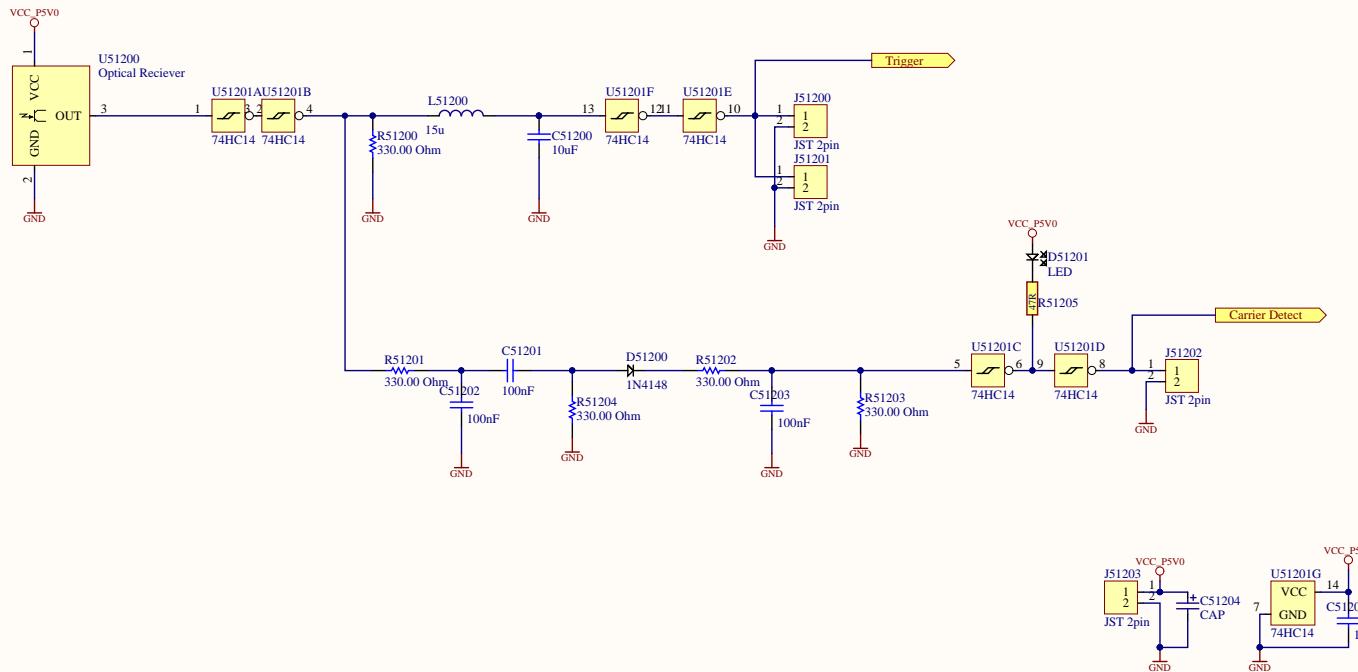

Title: TK512 Optisk Mottaker



Size: A3 Revision: 0 Author: Øystein Smith

Date: 26.04.2016 Sheet 6 of 20 Omega Verksted

File: D:\Temp\Tesla-Driver\05\_Hardware\TK500\_Driver\TK512\_Optisk\_Mottaker\TK512\_Optisk\_Mottaker.SchDoc

A

A

B


B

C

C

D


D

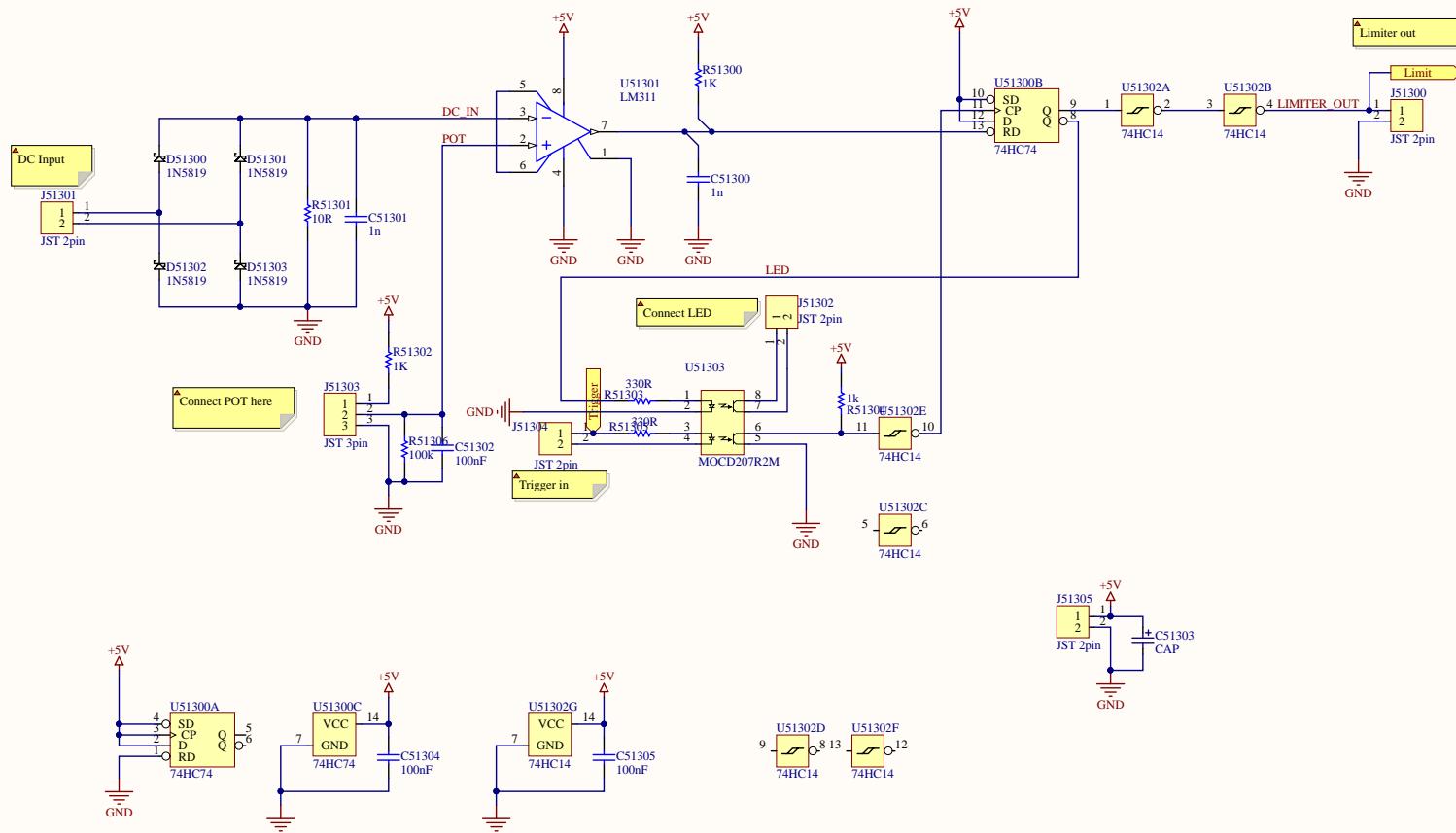

Title: TK513 Limiter



Size: A3	Revision: 0	Author: Øystein Smith
Date: 26.04.2016	Sheet 7 of 20	Omega Verksted
File: D:\Temp\Tesla-Driver\05_Hardware\TK500_Driver\TK513_Limiter\TK513_Limiter.SchDoc		

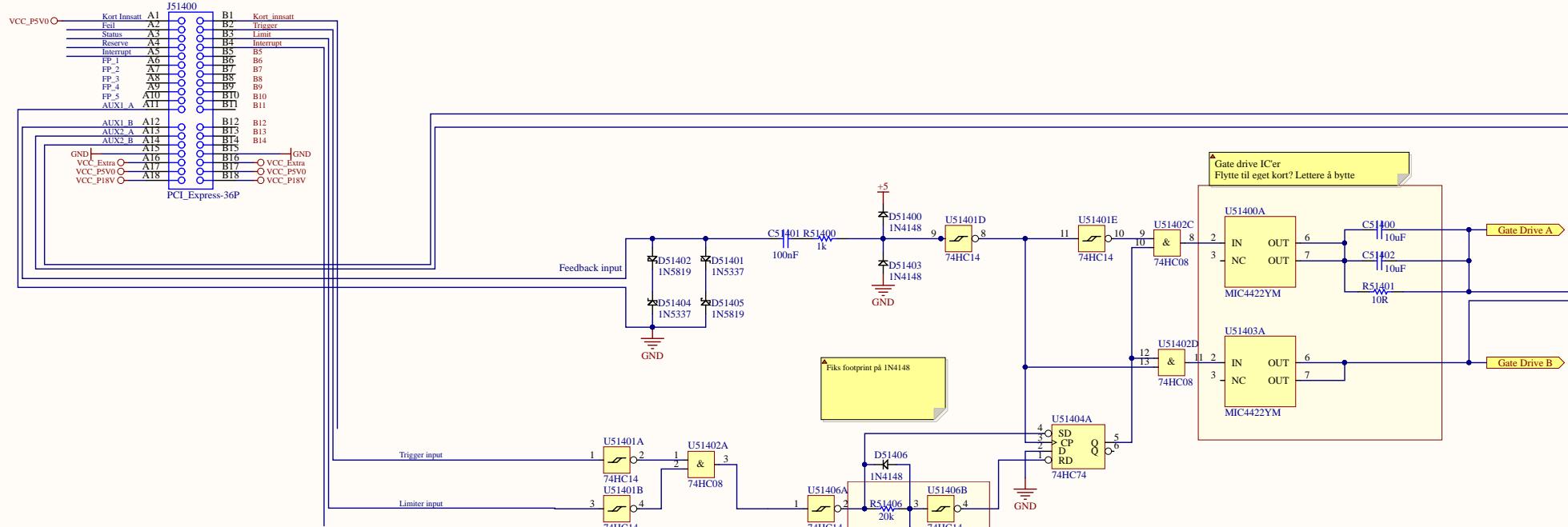

U51406D  
74HC14

U51406C  
74HC14  
GND

U51401F  
74HC14  
GND

U51406E  
74HC14  
GND

U51406F  
74HC14  
GND

U51404B  
74HC74  
10  
11  
12  
779  
779  
780  
781  
782  
783  
784  
785  
786  
787  
788  
789  
789  
790  
791  
792  
793  
794  
795  
796  
797  
798  
799  
800  
801  
802  
803  
804  
805  
806  
807  
808  
809  
809  
810  
811  
812  
813  
814  
815  
816  
817  
818  
819  
819  
820  
821  
822  
823  
824  
825  
826  
827  
828  
829  
829  
830  
831  
832  
833  
834  
835  
836  
837  
838  
839  
839  
840  
841  
842  
843  
844  
845  
846  
847  
848  
849  
849  
850  
851  
852  
853  
854  
855  
856  
857  
858  
859  
859  
860  
861  
862  
863  
864  
865  
866  
867  
868  
869  
869  
870  
871  
872  
873  
874  
875  
876  
877  
878  
879  
879  
880  
881  
882  
883  
884  
885  
886  
887  
888  
889  
889  
890  
891  
892  
893  
894  
895  
896  
897  
898  
899  
900  
901  
902  
903  
904  
905  
906  
907  
908  
909  
909  
910  
911  
912  
913  
914  
915  
916  
917  
918  
919  
919  
920  
921  
922  
923  
924  
925  
926  
927  
928  
929  
929  
930  
931  
932  
933  
934  
935  
936  
937  
938  
939  
939  
940  
941  
942  
943  
944  
945  
946  
947  
948  
949  
949  
950  
951  
952  
953  
954  
955  
956  
957  
958  
959  
959  
960  
961  
962  
963  
964  
965  
966  
967  
968  
969  
969  
970  
971  
972  
973  
974  
975  
976  
977  
978  
979  
979  
980  
981  
982  
983  
984  
985  
986  
987  
988  
989  
989  
990  
991  
992  
993  
994  
995  
996  
997  
998  
999  
1000  
1001  
1002  
1003  
1004  
1005  
1006  
1007  
1008  
1009  
1009  
1010  
1011  
1012  
1013  
1014  
1015  
1016  
1017  
1018  
1019  
1019  
1020  
1021  
1022  
1023  
1024  
1025  
1026  
1027  
1028  
1029  
1029  
1030  
1031  
1032  
1033  
1034  
1035  
1036  
1037  
1038  
1039  
1039  
1040  
1041  
1042  
1043  
1044  
1045  
1046  
1047  
1048  
1049  
1049  
1050  
1051  
1052  
1053  
1054  
1055  
1056  
1057  
1058  
1059  
1059  
1060  
1061  
1062  
1063  
1064  
1065  
1066  
1067  
1068  
1069  
1069  
1070  
1071  
1072  
1073  
1074  
1075  
1076  
1077  
1078  
1079  
1079  
1080  
1081  
1082  
1083  
1084  
1085  
1086  
1087  
1088  
1089  
1089  
1090  
1091  
1092  
1093  
1094  
1095  
1096  
1097  
1098  
1099  
1099  
1100  
1101  
1102  
1103  
1104  
1105  
1106  
1107  
1108  
1109  
1109  
1110  
1111  
1112  
1113  
1114  
1115  
1116  
1117  
1118  
1119  
1119  
1120  
1121  
1122  
1123  
1124  
1125  
1126  
1127  
1128  
1129  
1129  
1130  
1131  
1132  
1133  
1134  
1135  
1136  
1137  
1138  
1139  
1139  
1140  
1141  
1142  
1143  
1144  
1145  
1146  
1147  
1148  
1149  
1149  
1150  
1151  
1152  
1153  
1154  
1155  
1156  
1157  
1158  
1159  
1159  
1160  
1161  
1162  
1163  
1164  
1165  
1166  
1167  
1168  
1169  
1169  
1170  
1171  
1172  
1173  
1174  
1175  
1176  
1177  
1178  
1179  
1179  
1180  
1181  
1182  
1183  
1184  
1185  
1186  
1187  
1188  
1189  
1189  
1190  
1191  
1192  
1193  
1194  
1195  
1196  
1197  
1198  
1198  
1199  
1199  
1200  
1201  
1202  
1203  
1204  
1205  
1206  
1207  
1208  
1209  
1209  
1210  
1211  
1212  
1213  
1214  
1215  
1216  
1217  
1218  
1219  
1219  
1220  
1221  
1222  
1223  
1224  
1225  
1226  
1227  
1228  
1229  
1229  
1230  
1231  
1232  
1233  
1234  
1235  
1236  
1237  
1238  
1239  
1239  
1240  
1241  
1242  
1243  
1244  
1245  
1246  
1247  
1248  
1249  
1249  
1250  
1251  
1252  
1253  
1254  
1255  
1256  
1257  
1258  
1259  
1259  
1260  
1261  
1262  
1263  
1264  
1265  
1266  
1267  
1268  
1269  
1269  
1270  
1271  
1272  
1273  
1274  
1275  
1276  
1277  
1278  
1279  
1279  
1280  
1281  
1282  
1283  
1284  
1285  
1286  
1287  
1288  
1289  
1289  
1290  
1291  
1292  
1293  
1294  
1295  
1296  
1297  
1298  
1298  
1299  
1299  
1300  
1301  
1302  
1303  
1304  
1305  
1306  
1307  
1308  
1309  
1309  
1310  
1311  
1312  
1313  
1314  
1315  
1316  
1317  
1318  
1319  
1319  
1320  
1321  
1322  
1323  
1324  
1325  
1326  
1327  
1328  
1329  
1329  
1330  
1331  
1332  
1333  
1334  
1335  
1336  
1337  
1338  
1339  
1339  
1340  
1341  
1342  
1343  
1344  
1345  
1346  
1347  
1348  
1349  
1349  
1350  
1351  
1352  
1353  
1354  
1355  
1356  
1357  
1358  
1359  
1359  
1360  
1361  
1362  
1363  
1364  
1365  
1366  
1367  
1368  
1369  
1369  
1370  
1371  
1372  
1373  
1374  
1375  
1376  
1377  
1378  
1379  
1379  
1380  
1381  
1382  
1383  
1384  
1385  
1386  
1387  
1388  
1389  
1389  
1390  
1391  
1392  
1393  
1394  
1395  
1396  
1397  
1398  
1398  
1399  
1399  
1400  
1401  
1402  
1403  
1404  
1405  
1406  
1407  
1408  
1409  
1409  
1410  
1411  
1412  
1413  
1414  
1415  
1416  
1417  
1418  
1419  
1419  
1420  
1421  
1422  
1423  
1424  
1425  
1426  
1427  
1428  
1429  
1429  
1430  
1431  
1432  
1433  
1434  
1435  
1436  
1437  
1438  
1439  
1439  
1440  
1441  
1442  
1443  
1444  
1445  
1446  
1447  
1448  
1449  
1449  
1450  
1451  
1452  
1453  
1454  
1455  
1456  
1457  
1458  
1459  
1459  
1460  
1461  
1462  
1463  
1464  
1465  
1466  
1467  
1468  
1469  
1469  
1470  
1471  
1472  
1473  
1474  
1475  
1476  
1477  
1478  
1479  
1479  
1480  
1481  
1482  
1483  
1484  
1485  
1486  
1487  
1488  
1489  
1489  
1490  
1491  
1492  
1493  
1494  
1495  
1496  
1497  
1498  
1498  
1499  
1499  
1500  
1501  
1502  
1503  
1504  
1505  
1506  
1507  
1508  
1509  
1509  
1510  
1511  
1512  
1513  
1514  
1515  
1516  
1517  
1518  
1519  
1519  
1520  
1521  
1522  
1523  
1524  
1525  
1526  
1527  
1528  
1529  
1529  
1530  
1531  
1532  
1533  
1534  
1535  
1536  
1537  
1538  
1539  
1539  
1540  
1541  
1542  
1543  
1544  
1545  
1546  
1547  
1548  
1549  
1549  
1550  
1551  
1552  
1553  
1554  
1555  
1556  
1557  
1558  
1559  
1559  
1560  
1561  
1562  
1563  
1564  
1565  
1566  
1567  
1568  
1569  
1569  
1570  
1571  
1572  
1573  
1574  
1575  
1576  
1577  
1578  
1579  
1579  
1580  
1581  
1582  
1583  
1584  
1585  
1586  
1587  
1588  
1589  
1589  
1590  
1591  
1592  
1593  
1594  
1595  
1596  
1597  
1598  
1598  
1599  
1599  
1600  
1601  
1602  
1603  
1604  
1605  
1606  
1607  
1608  
1609  
1609  
1610  
1611  
1612  
1613  
1614  
1615  
1616  
1617  
1618  
1619  
1619  
1620  
1621  
1622  
1623  
1624  
1625  
1626  
1627  
1628  
1629  
1629  
1630  
1631  
1632  
1633  
1634  
1635  
1636  
1637  
1638  
1639  
1639  
1640  
1641  
1642  
1643  
1644  
1645  
1646  
1647  
1648  
1649  
1649  
1650  
1651  
1652  
1653  
1654  
1655  
1656  
1657  
1658  
1659  
1659  
1660  
1661  
1662  
1663  
1664  
1665  
1666  
1667  
1668  
1669  
1669  
1670  
1671  
1672  
1673  
1674  
1675  
1676  
1677  
1678  
1679  
1679  
1680  
1681  
1682  
1683  
1684  
1685  
1686  
1687  
1688  
1689  
1689  
1690  
1691  
1692  
1693  
1694  
1695  
1696  
1697  
1698  
1698  
1699  
1699  
1700  
1701  
1702  
1703  
1704  
1705  
1706  
1707  
1708  
1709  
1709  
1710  
1711  
1712  
1713  
1714  
1715  
1716  
1717  
1718  
1719  
1719  
1720  
1721  
1722  
1723  
1724  
1725  
1726  
1727  
1728  
1729  
1729  
1730  
1731  
1732  
1733  
1734  
1735  
1736  
1737  
1738  
1739  
1739  
1740  
1741  
1742  
1743  
1744  
1745  
1746  
1747  
1748  
1749  
1749  
1750  
1751  
1752  
1753  
1754  
1755  
1756  
1757  
1758  
1759  
1759  
176

A

A

B



B

C

C

D

D

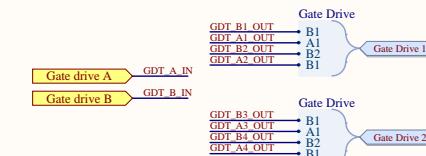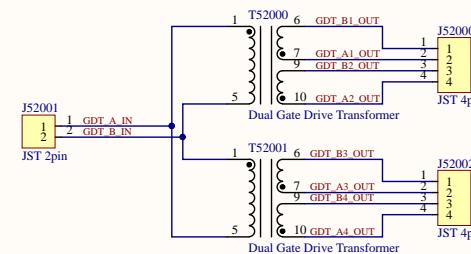

Title: TK520 GDT-Trafo



Size: A3	Revision: 1	Author: Øystein Smith
Date: 26.04.2016	Sheet 13 of 20	Omega Verksted
File: D:\Temp\Tesla-Driver\05_Hardware\TK500_Driver\TK520_GDT-Trafo\TK520_GDT-Trafo.SchDoc		

A

A

B


B

C

C

D

D

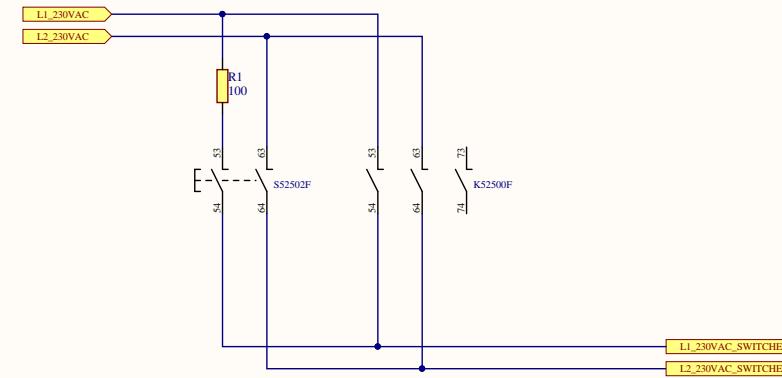

Title: TK525 Hovedstrøm



Size: A3 | Revision: 0 | Author: Øystein Smith

Date: 26.04.2016 | Sheet 14 of 20 | Omega Verksted

File: D:\Temp\Tesla-Driver\05\_Hardware\TK500\_Driver\TK525\_Hovedstrom.SchDoc

A

A

B


B

C

C

D

D

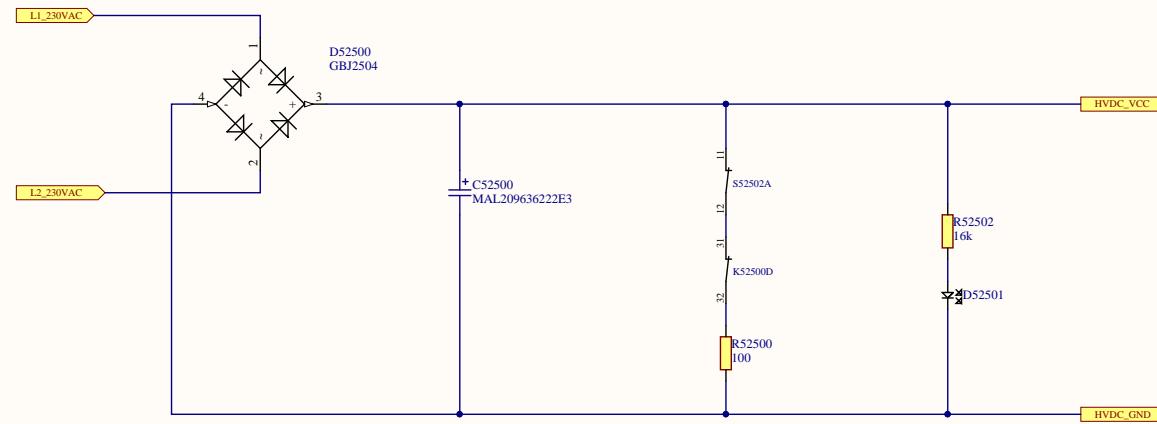

Title: TK525 HVDC



Size: A3 Revision: 0 Author: Øystein Smith

Date: 26.04.2016 Sheet 15 of 20 Omega Verksted

File: D:\Temp\Tesla-Driver\05\_Hardware\TK500\_Driver\TK525\_HVDC.SchDoc

A

A

B


B

C

C

D

D

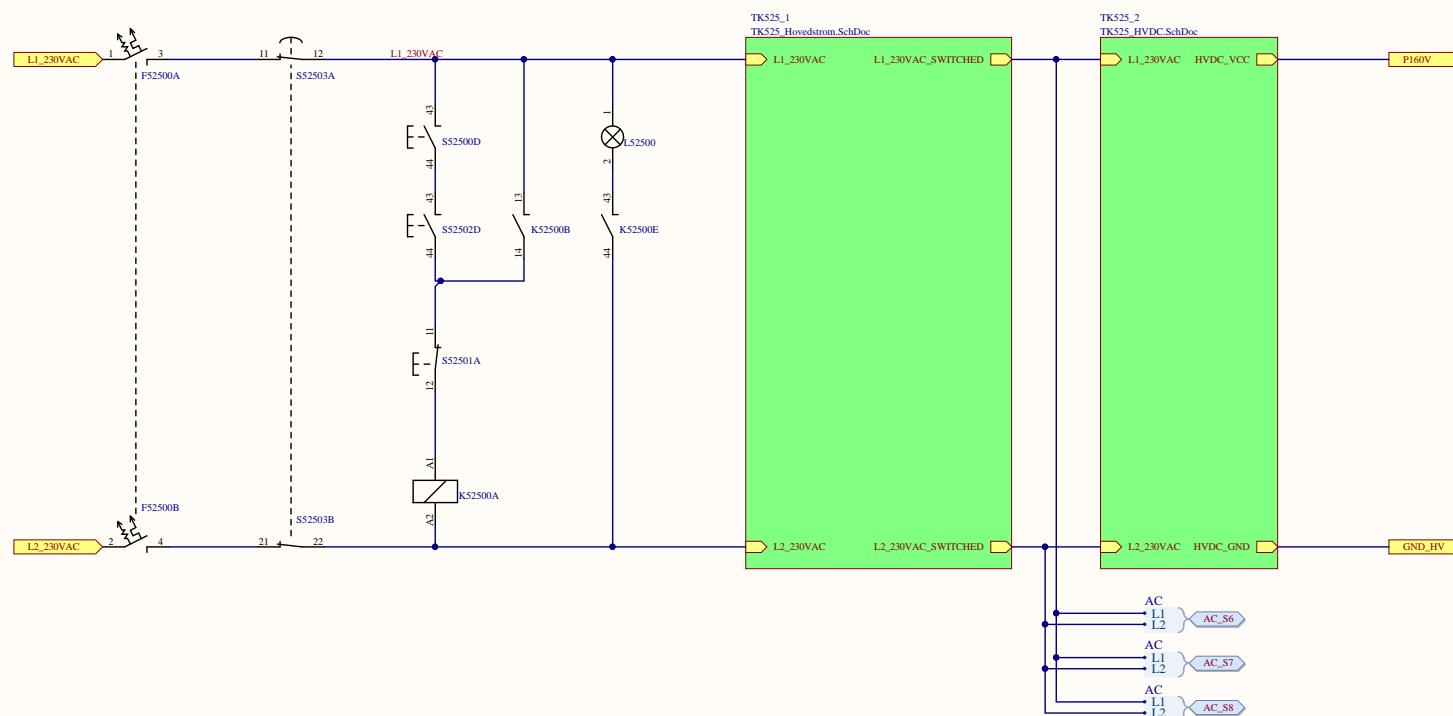


Title: TK525 Kraftforsyning



Size: A3 Revision: 0 Author: Øystein Smith

Date: 26.04.2016 Sheet 16 of 20 Omega Verksted

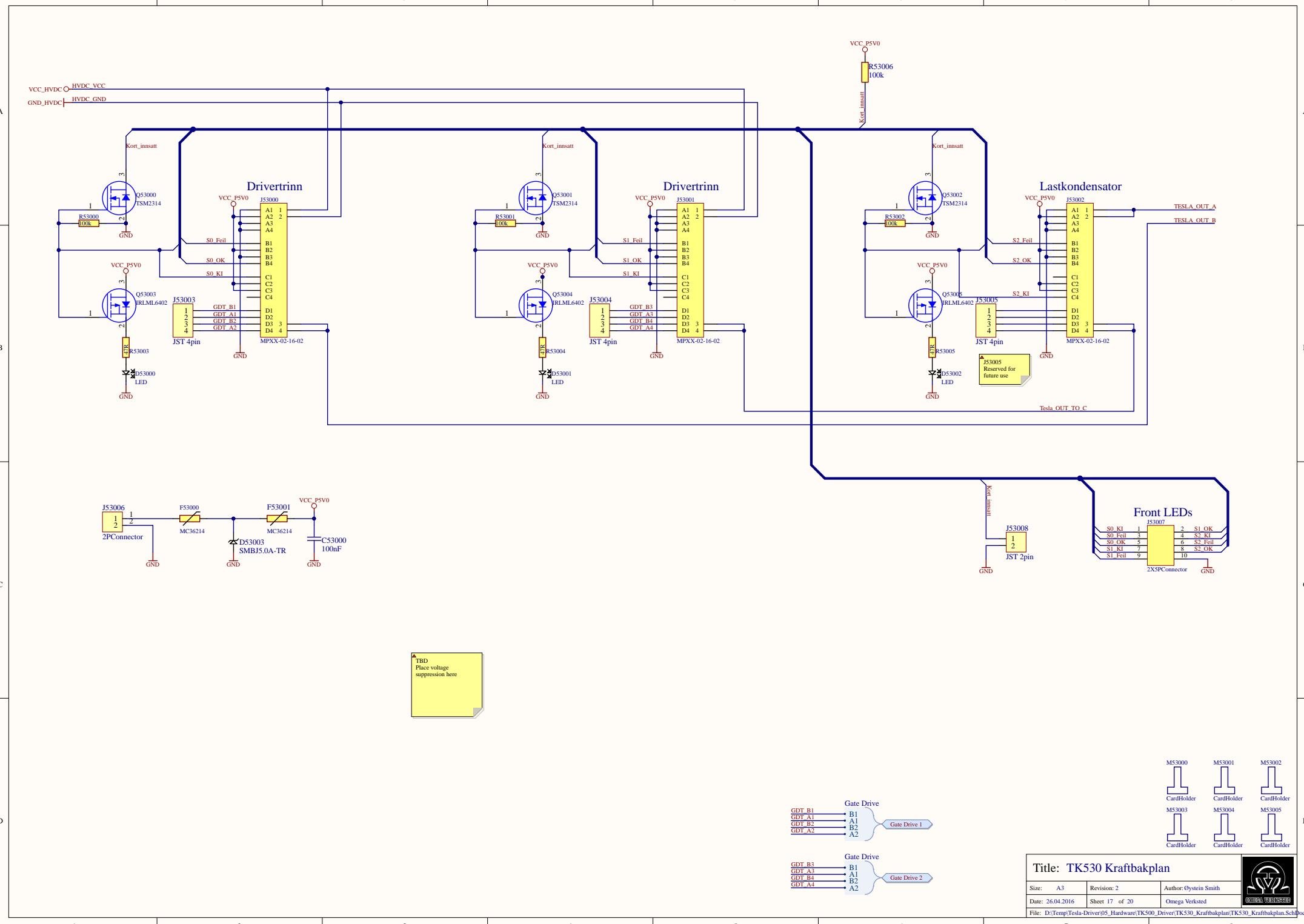File: D:\Temp\Tesla-Driver\05\_Hardware\TK500\_Driver\TK525\_Kraftforsyning.SchDoc



A

A

B


B

C

C

D

D

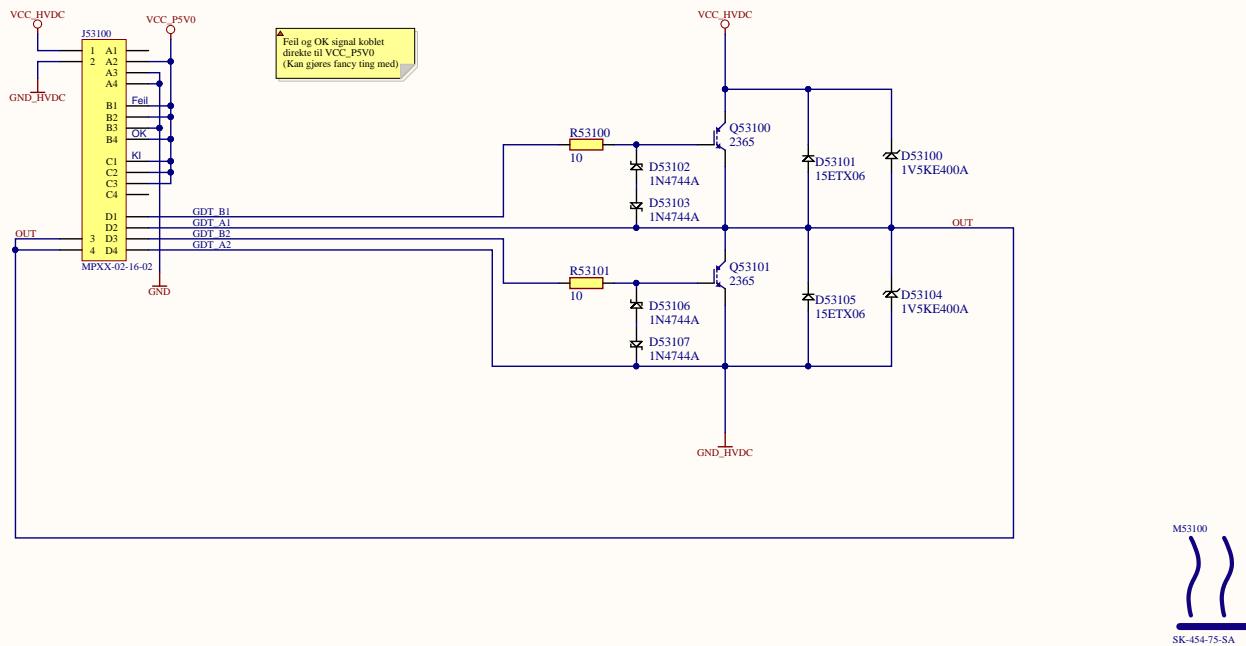

Title: TK531 Utgangstrinn



Size: A3 Revision: 2 Author: Øystein Smith

Date: 26.04.2016 Sheet 18 of 20 Omega Verksted


File: D:\Temp\Tesla-Driver\05\_Hardware\TK500\_Driver\TK531\_Utgangstrinn\TK531\_Utgangstrinn.SchDoc

A

A

B

B

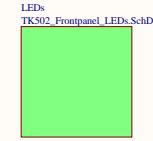

C

C

D

D

Title: TK540 Frontpanel



Size: A3	Revision: 0	Author: *
Date: 26.04.2016	Sheet 20 of 20	Omega Verksted
File: D:\Temp\Tesla-Driver\05_Hardware\TK500_Driver\TK540_Frontpanel.SchDoc		

A

A

B


B

C

C

D

D

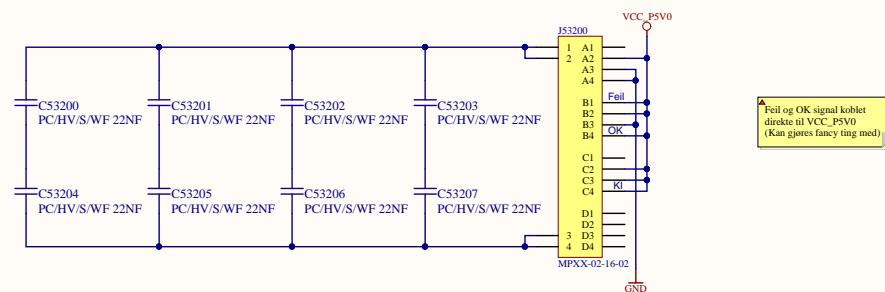

Title: TK532 Kondensatorkort



Size: A3 Revision: 2 Author: Øystein Smith

Date: 26.04.2016 Sheet \* of \* Omega Verksted

File: D:\Temp\Tesla-Driver\05\_Hardware\TK500\_Driver\TK532\_Kondensatorkort\TK532\_Kondensatorkort.SchDoc

## **C Layout**


This page is intentionally left (almost) blank.


# Portable and reliable DRSSTC demonstrator


C.1 TK510


C LAYOUT

C.1 TK510

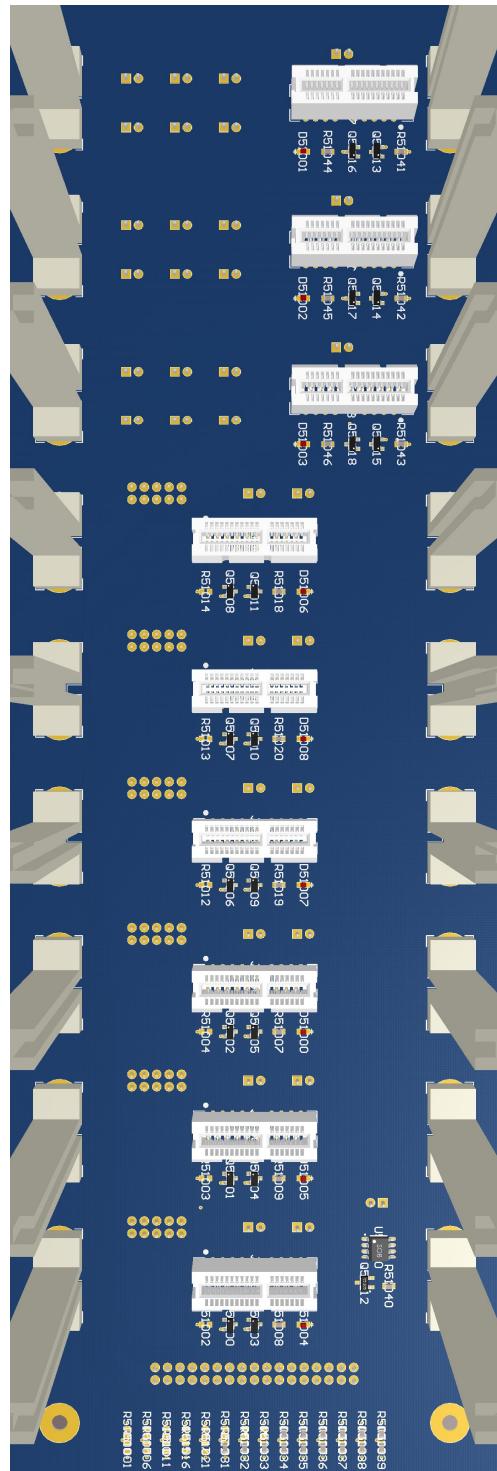


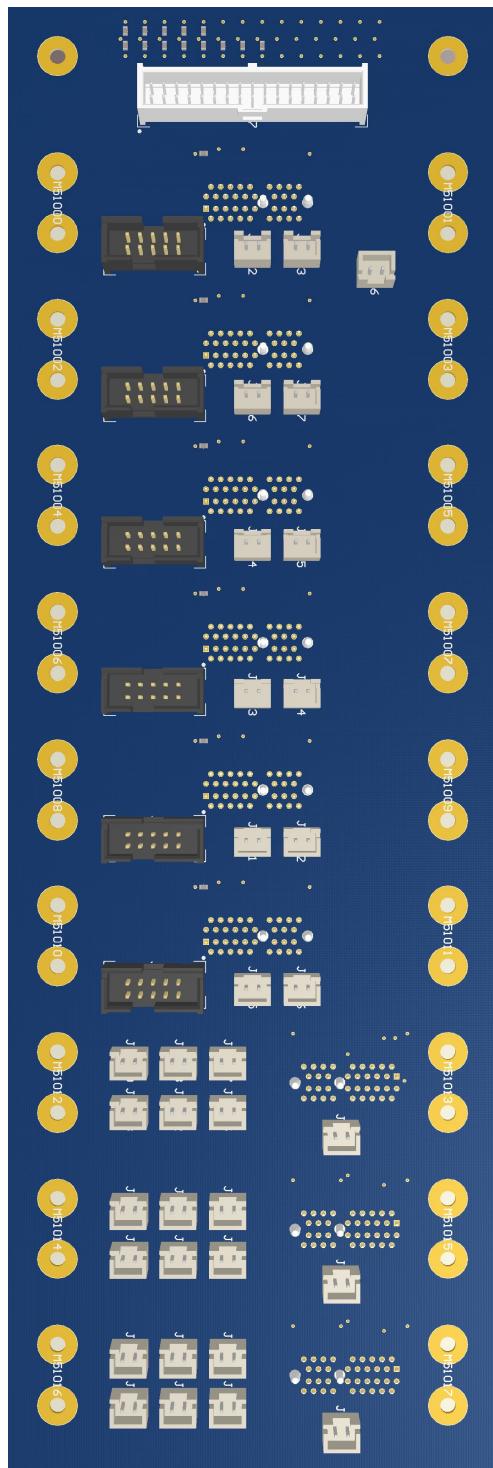


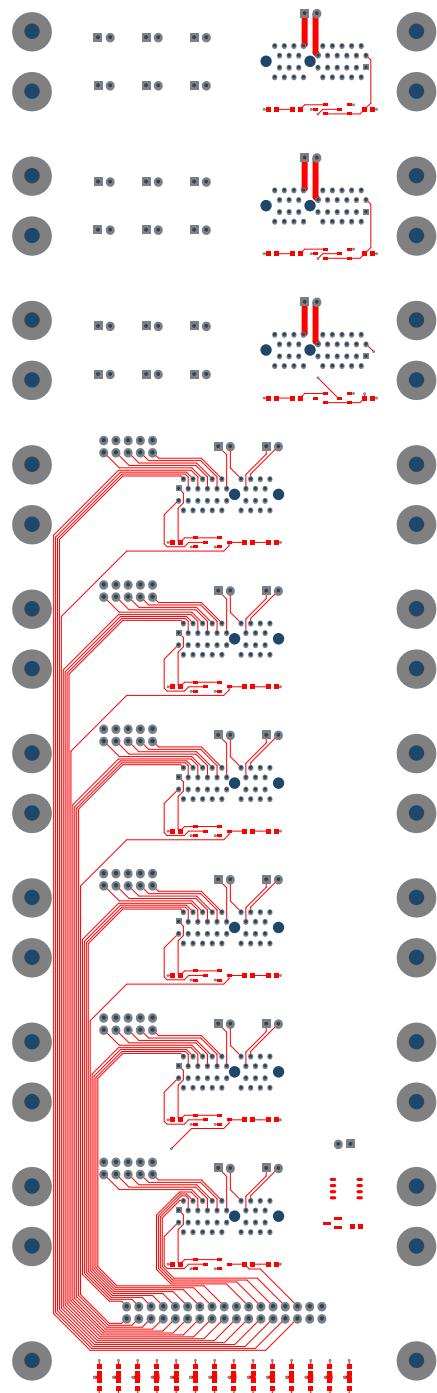

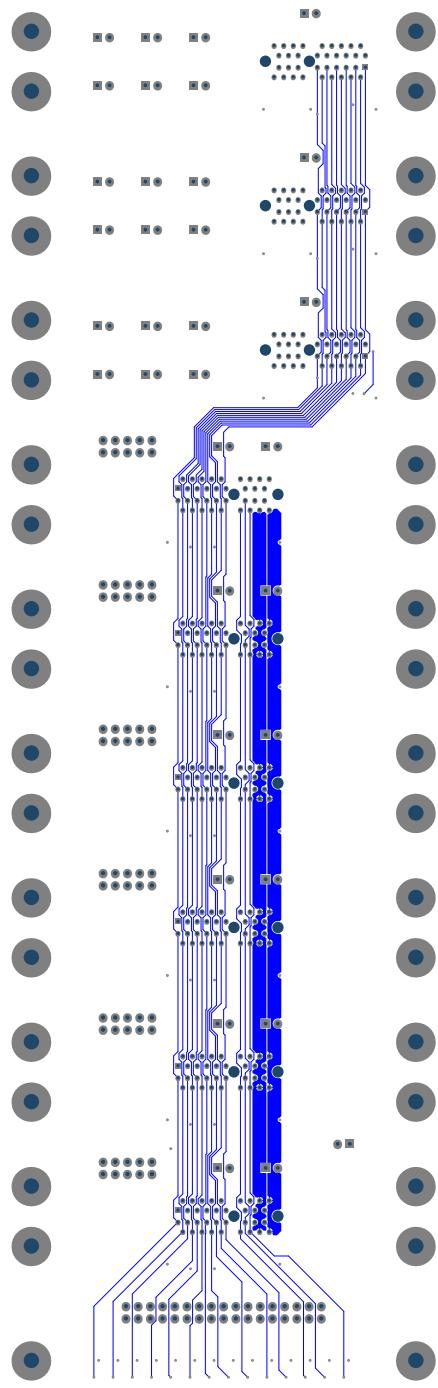



## C.2 TK511

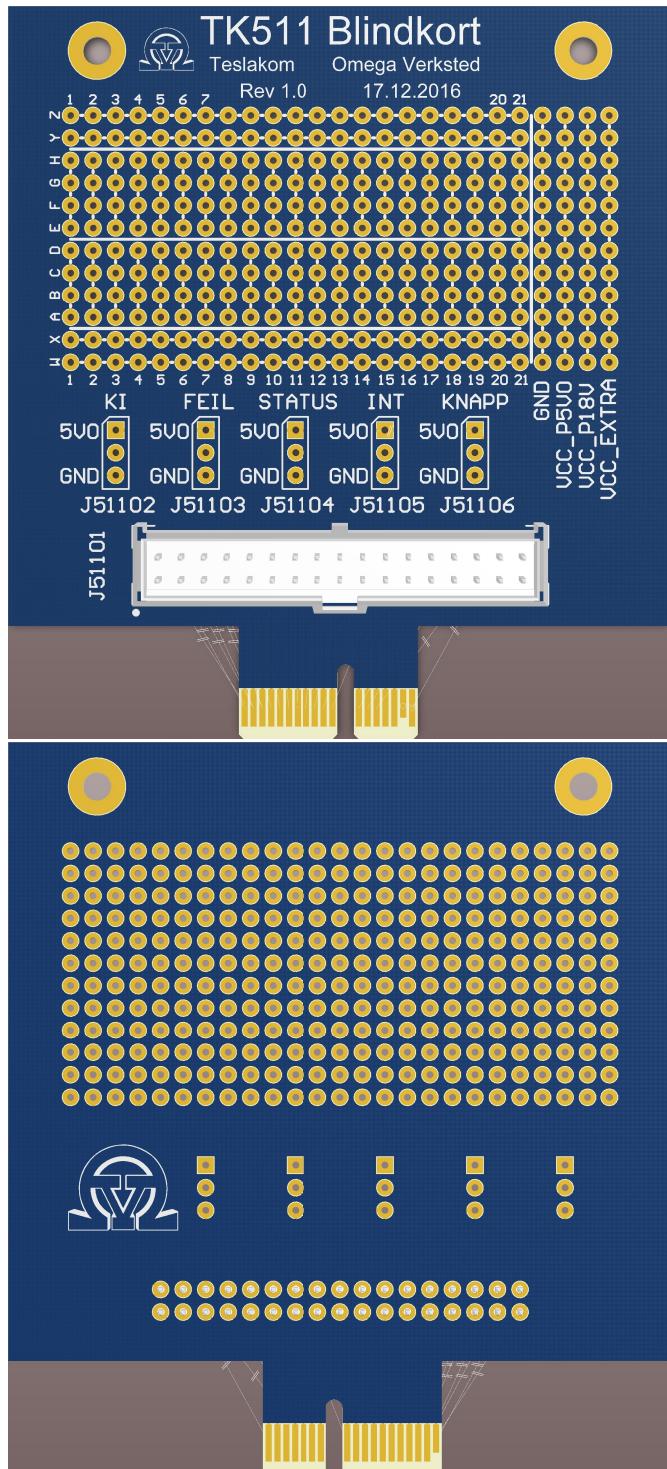

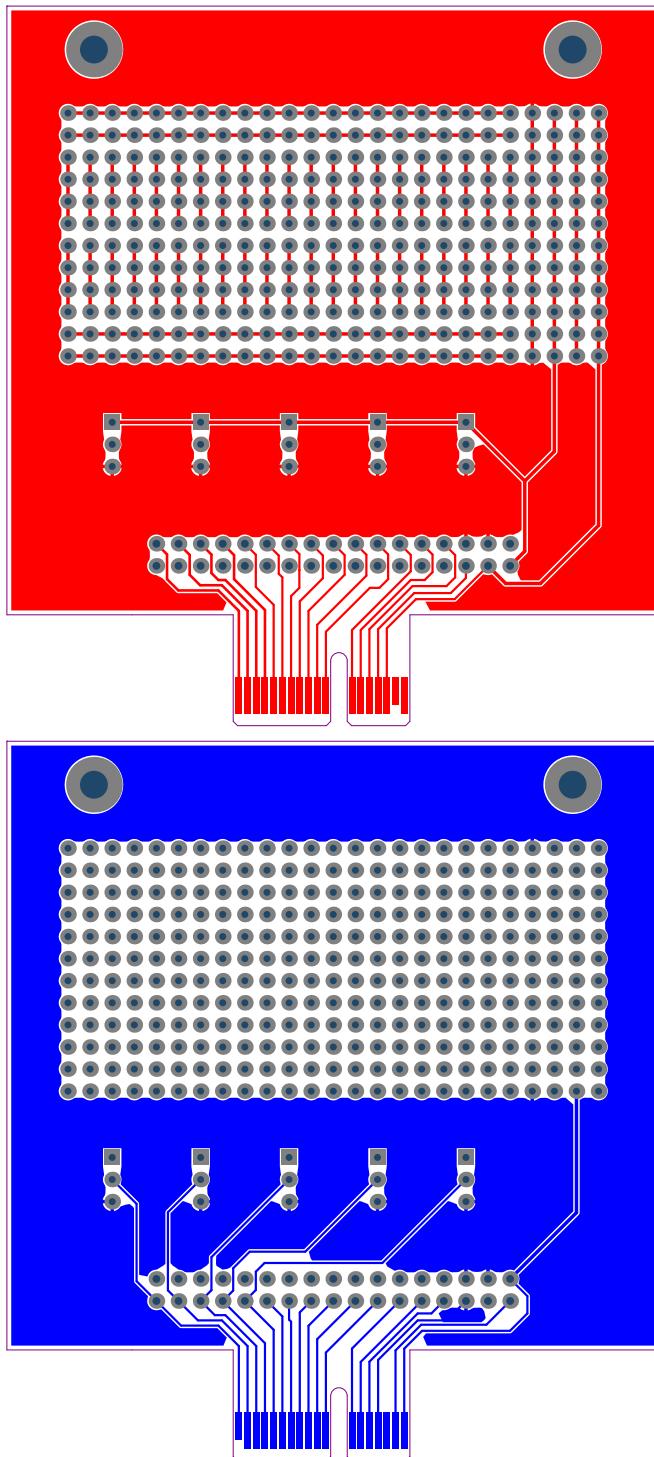



### C.3 TK520

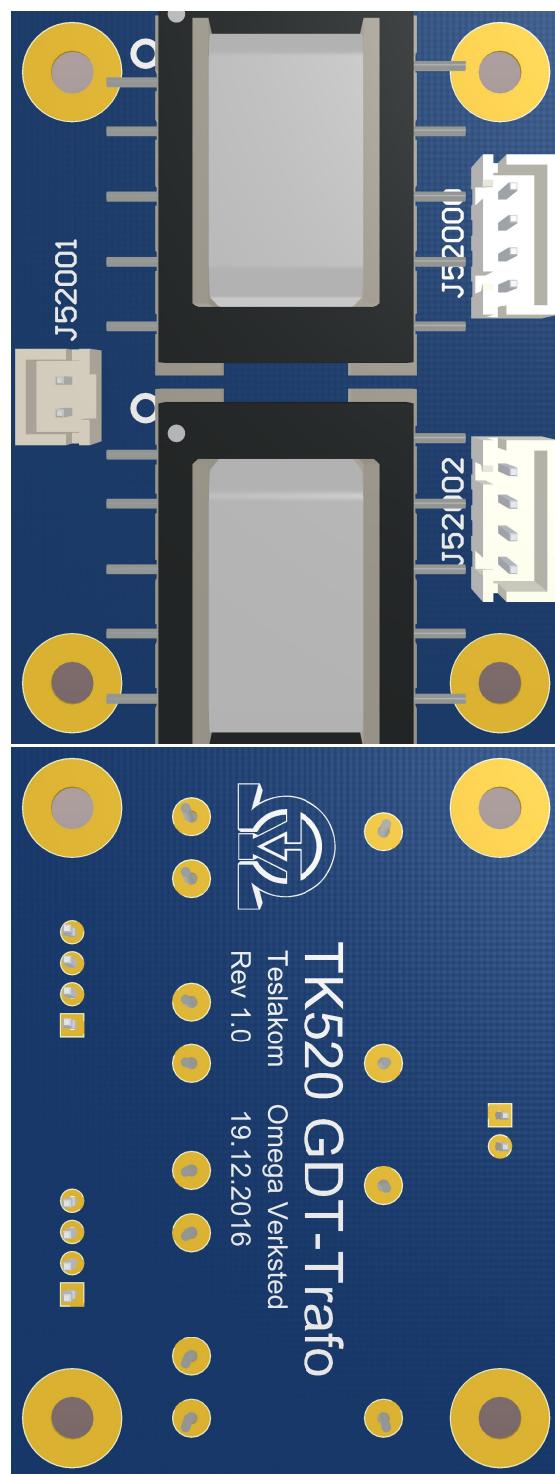


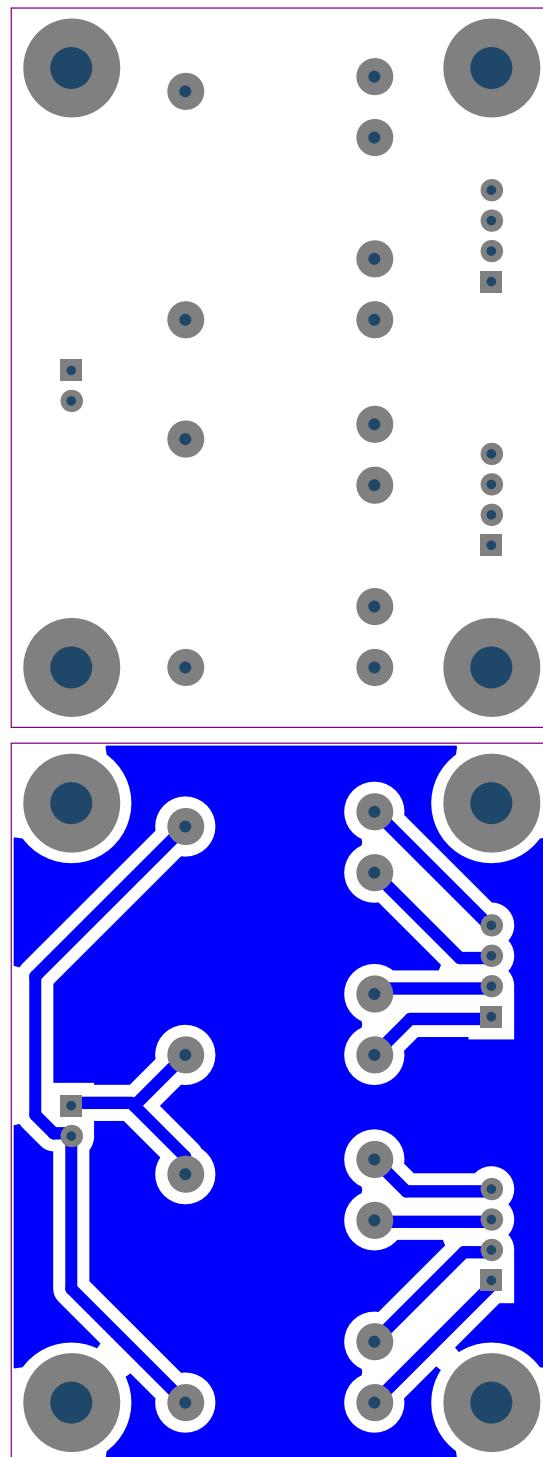


## C.4 TK530

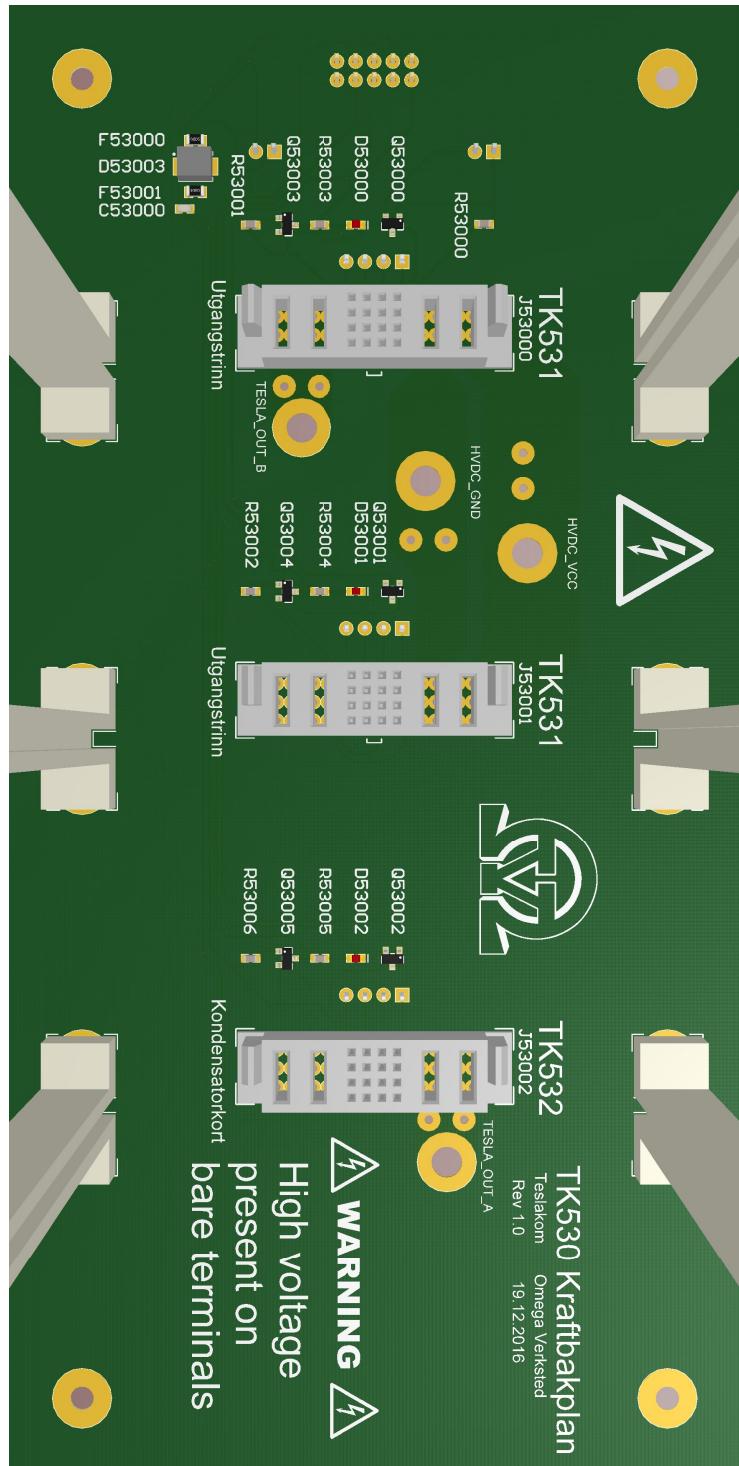


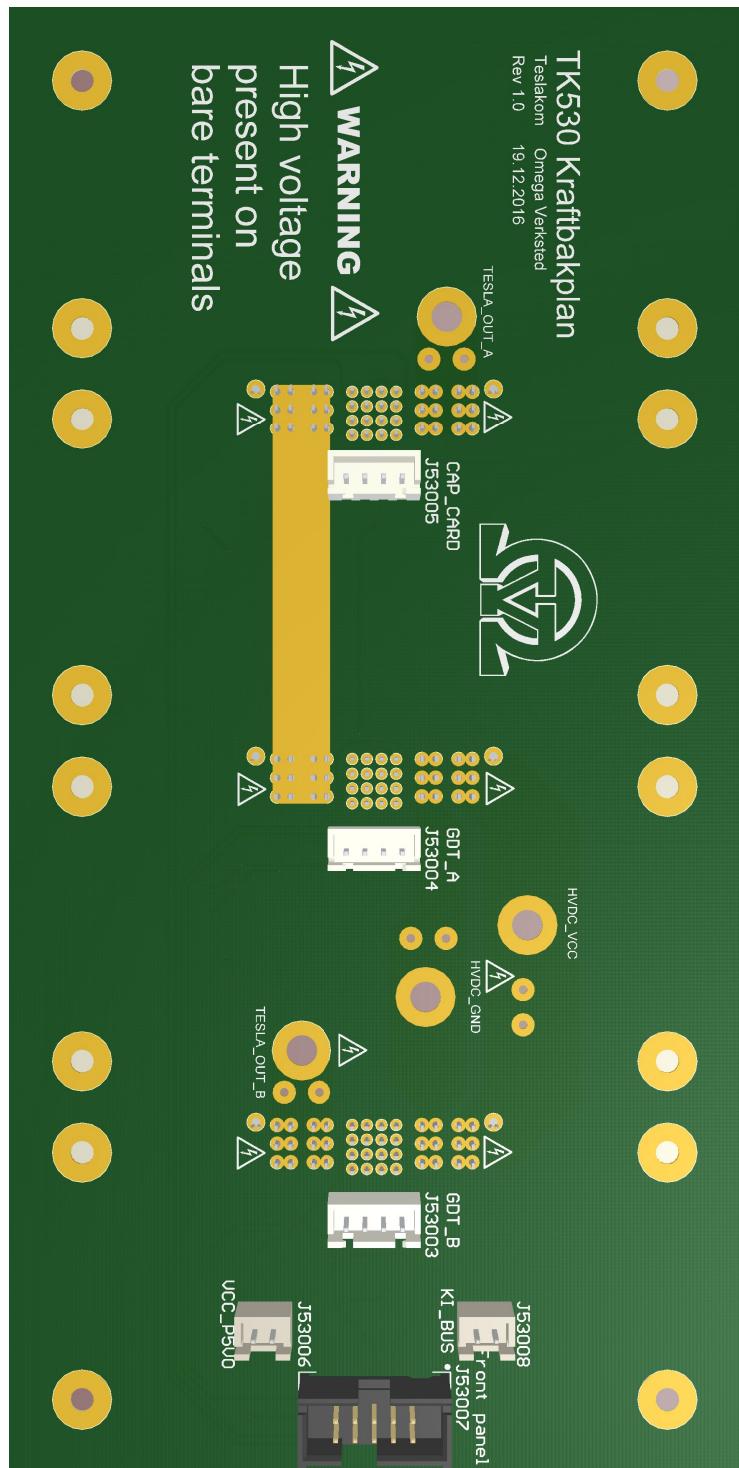


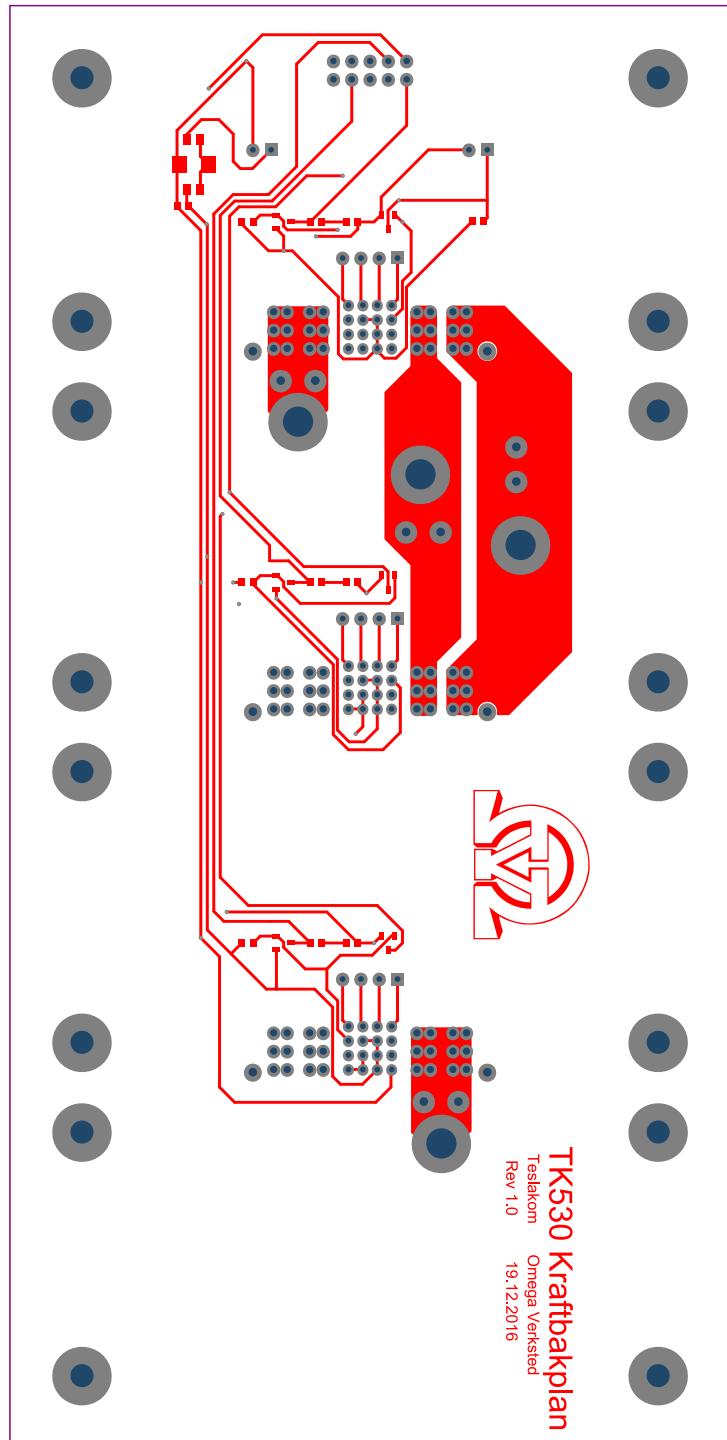

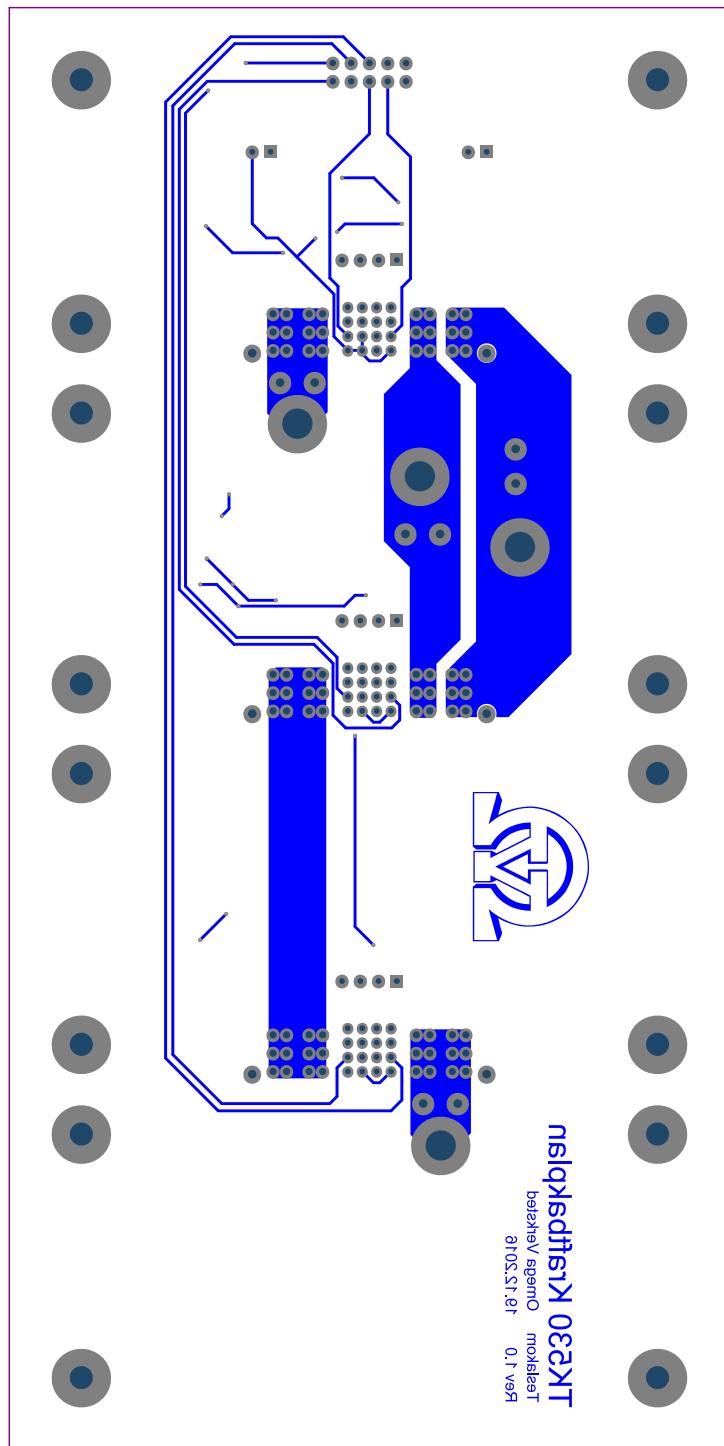

## C.5 TK531

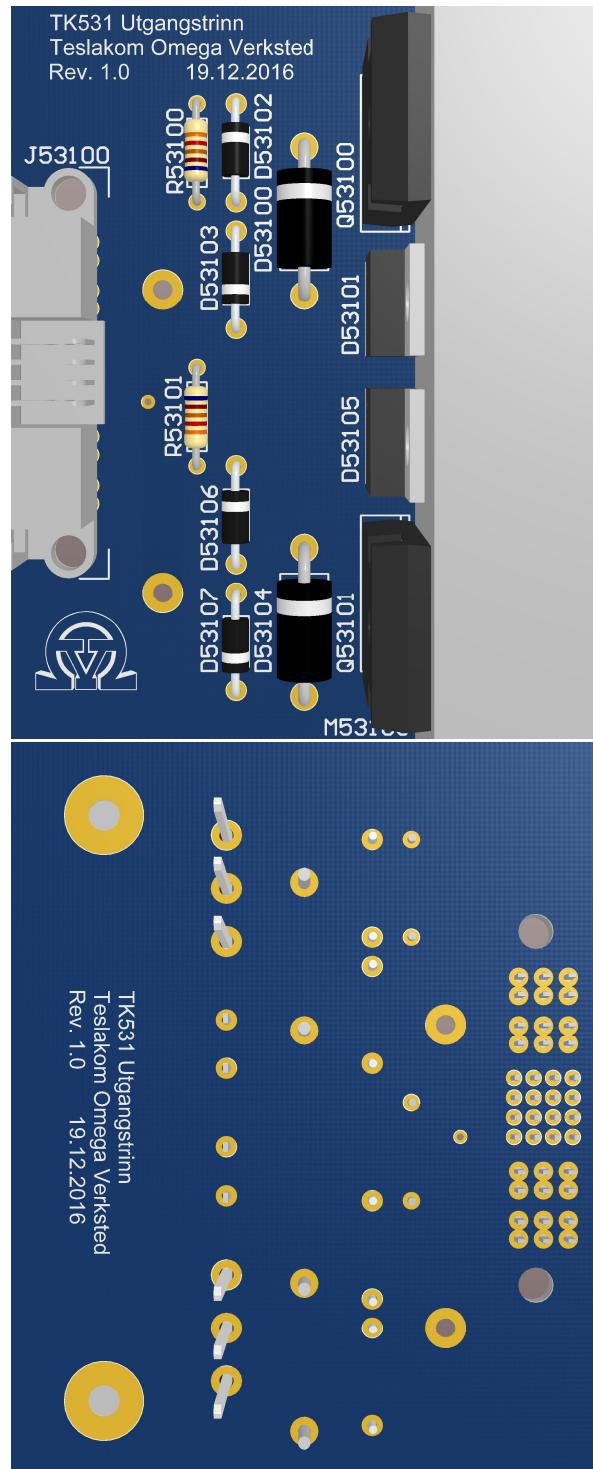

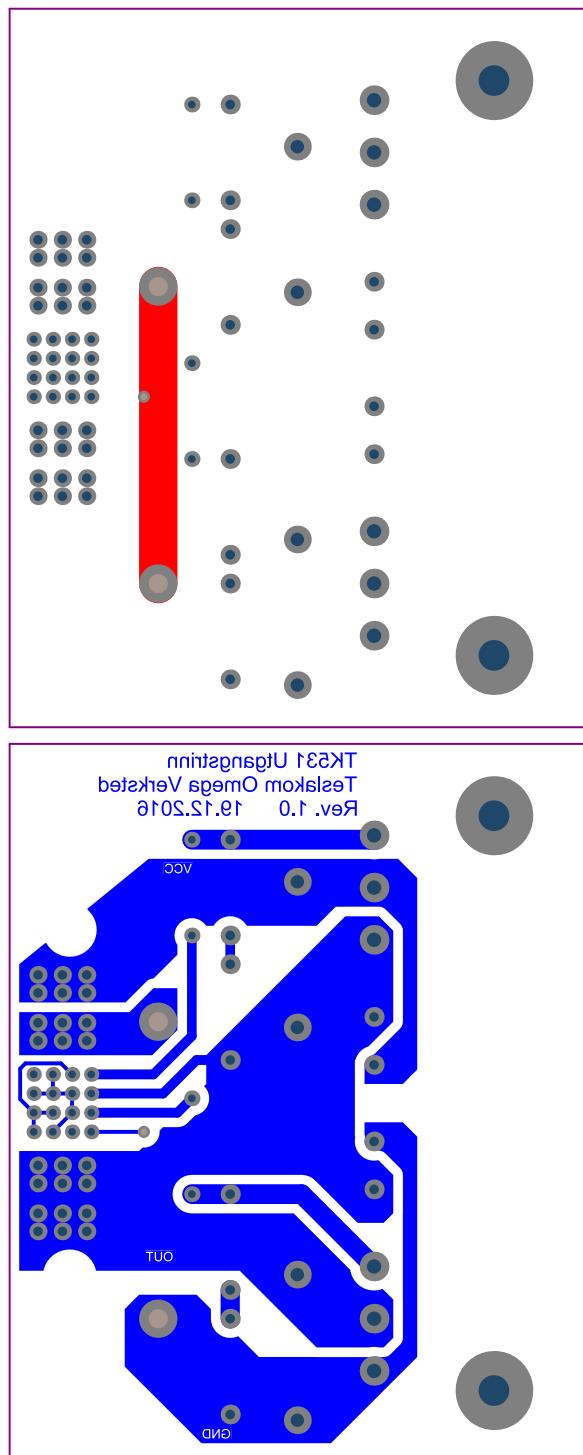

## C.6 TK532

